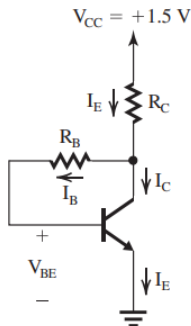


5.1:

Solution:



(a) For the dc analysis, refer to the figure:

$$V_{CC} = I_E R_C + I_B R_B + V_{BE} \rightarrow 1.5 = I_E \times 1 + \frac{I_E}{\beta + 1} \times 47 + 0.7 \rightarrow I_E = \frac{1.5 - 0.7}{1 + \frac{47}{101}} = 0.546 \text{ mA}$$

$$I_C = \alpha I_E = 0.99 \times 0.546 = 0.54 \text{ mA}$$

(b) $g_m = \frac{I_C}{V_T} = \frac{0.54 \text{ mA}}{0.025 \text{ V}} = 21.6 \text{ mA/V}$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{21.6} = 4.63 \text{ k}\Omega$$


(c) $\frac{V_o}{V_b} = -g_m(R_C || R_L) = -21.6(1 || 1) = -10.8 \text{ V}$

(d) Using Miller's theorem, the component of R_{in} due to R_B can be found as:

$$R_{in1} = \frac{R_B}{1 - \left(\frac{V_o}{V_b}\right)} = \frac{47 \text{ k}\Omega}{1 - (-10.8)} = 4 \text{ k}\Omega$$

$$R_{in} = R_{in1} || r_\pi = 4 || 4.63 = 2.14 \text{ k}\Omega$$

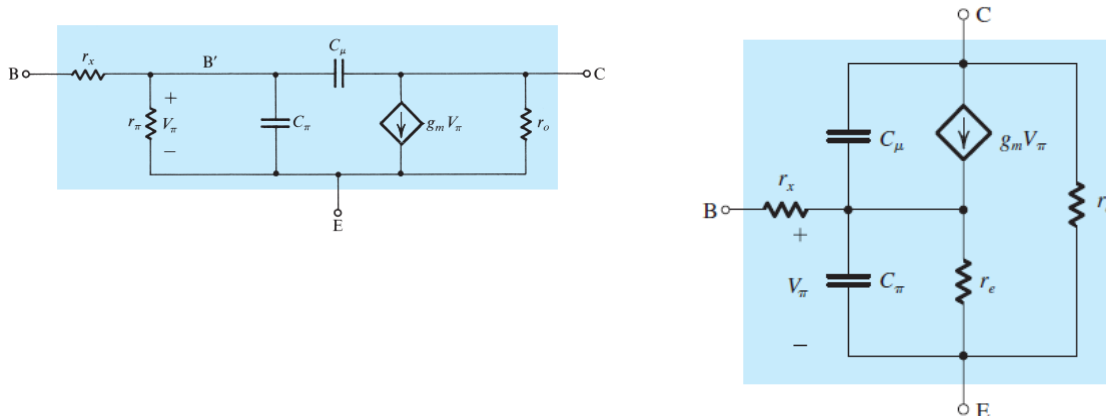(e) $G_V = \frac{R_{in}}{R_{in} + R_{sig}} \times \frac{V_o}{V_b} = \frac{2.14}{1 + 2.14} \times -10.8 = -7.4$



$$(f) C_{in} = C_{\pi} + (1 + | \frac{V_o}{V_b} |) C_{\mu}$$

Where:

$$C_{\pi} + C_{\mu} = \frac{g_m}{2\pi f_T} = \frac{21.6 \times 10^{-3}}{2\pi \times 600 \times 10^6} = 5.73 \text{ pF}$$

$$C_{\pi} = 5.73 - 0.8 = 4.93 \text{ pF}$$




$$C_{in} = 4.93 + (1 + 10.8) \times 0.8 = 14.37 \text{ pF}$$

$$(g) R'_{sig} = R_{in} \parallel R_{sig} = 214 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 0.68 \text{ k}\Omega$$

$$f_H = \frac{1}{2\pi C_{in} R'_{sig}} = \frac{1}{2\pi \times 14.37 \times 10^{-12} \times 0.68 \times 10^3} = 16.3 \text{ MHz}$$

5.2:

Solution:

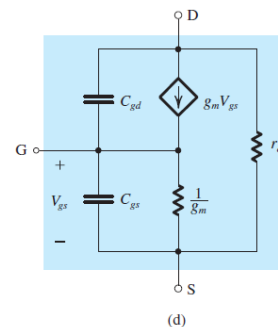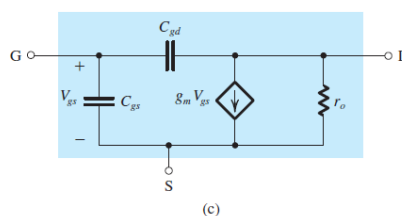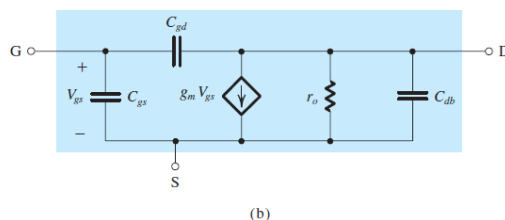

Since the total resistance at the drain is r_o , we have:

$$A_M = -g_m r_o$$

$$\tau_{gs} = C_{gs} R_{gs} = C_{gs} R_{sig}$$

$$R_{gd} = R_{sig} (1 + g_m r_o) + r_o$$

$$\tau_{gd} = C_{gd} R_{gd} = C_{gd} [R_{sig} (1 + g_m r_o) + r_o]$$

$$\tau_{cL} = C_L R'_L = C_L r_o$$

Thus,

$$\tau_H = \tau_{cL} + \tau_{gd} + \tau_{cs} = C_{gs} R_{sig} + C_{gd} [R_{sig} (1 + g_m r_o) + r_o] + C_L r_o$$

For the given numerical values:

$$A_M = -1 \times 20 = -20$$

$$\tau_H = 20 \times 20 + 5[20(1 + 1 \times 20) + 20] + 10 \times 20 = 400 + 2200 + 200 = 2800 \text{ ps}$$


$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 2.8 \times 10^{-9}} = 56.8 \text{ MHz}$$

$$GB = 20 \times 56.8 = 1.14 \text{ GHz}$$

Assignment Project Exam Help

(b)

<https://powcoder.com>

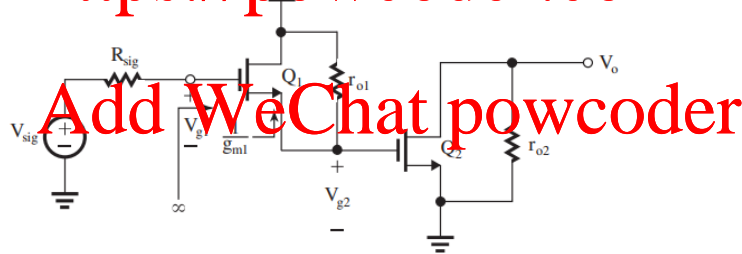

We see that:

$$\frac{V_{g1}}{V_{sig}} = 1, \quad \frac{V_{g2}}{V_{g1}} = \frac{r_{o1}}{\frac{1}{g_{m1}} + r_{o1}}, \quad \frac{V_o}{V_{g2}} = -g_{m2} r_{o2}$$

$$A_M = 1 \times \frac{r_{o1}}{\frac{1}{g_{m1}} + r_{o1}} \times -g_{m2} r_{o2} = -\frac{r_{o1}}{\frac{1}{g_{m1}} + r_{o1}} (g_{m2} r_{o2})$$

Next, we evaluate the open-circuit time constants. Refer to Figure 2:

C_{gd1} : Capacitor C_{gd1} is between G_1 and ground and thus sees the resistance R_{sig} ,

$$R_{gd1} = R_{sig}$$

$$\tau_{gd1} = C_{gd1}R_{sig}$$

C_{gs1} : To find the resistance R_{gs1} seen by capacitor C_{gs1} , we replace Q_1 with its hybrid- π equivalent circuit with V_{sig} set to zero, $C_{gd1} = 0$ and C_{gs1} replaced by a test voltage V_x . The resulting equivalent circuit is shown in the figure 3:

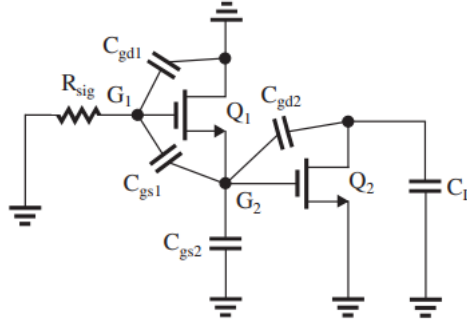


Figure 2

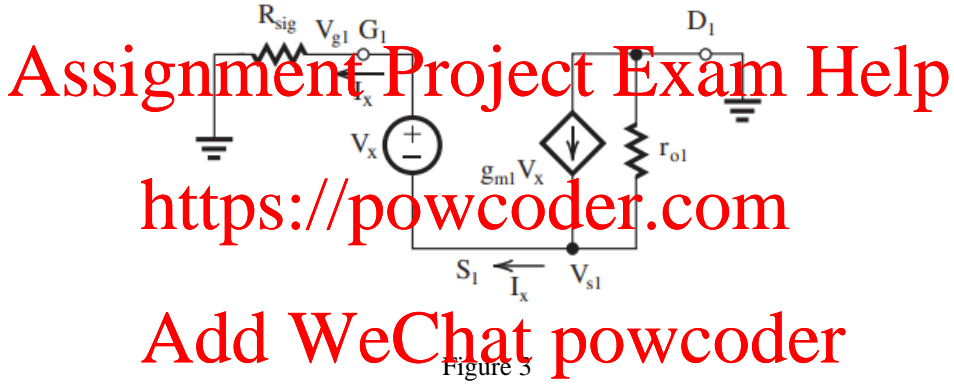


Figure 3

Analysis of the circuit in figure 3 proceeds as follows:

$$V_{g1} = I_X R_{sig}$$

$$V_{s1} = V_{g1} - V_X = I_X R_{sig} - V_X$$

At S_1 :

$$I_X = g_{m1} V_X - \frac{V_{S1}}{r_{o1}} = g_{m1} V_X - \frac{I_X R_{sig} - V_X}{r_{o1}} \rightarrow I_X \left(1 + \frac{R_{sig}}{r_{o1}} \right) = V_X \left(g_{m1} + \frac{1}{r_{o1}} \right)$$

$$R_{gs1} = \frac{V_X}{I_X} = \frac{R_{sig} + r_{o1}}{1 + g_{m1} r_{o1}}$$

$$\tau_{gs1} = C_{gs1} \frac{R_{sig} + r_{o1}}{1 + g_{m1}r_{o1}}$$

C_{gs2} : Capacitor C_{gs2} sees the resistance between G_2 and ground, which is the output resistance of source follower Q_1

$$R_{gs2} = \frac{1}{g_{m1}} || r_{o1}$$

Thus,

$$\tau_{gs2} = C_{gs2} \left(\frac{1}{g_{m1}} || r_{o1} \right)$$

C_{gs2} : Transistor Q_2 operates as a CS amplifier with an equivalent signal-source resistance equal to the output resistance of the source follower Q_1 , that is $\frac{1}{g_{m1}} || r_{o1}$ and with a gain from gate to drain of $g_{m2}r_{o2}$.

Thus, the formula for R_{gd} in a CS amplifier can be adapted as follows:

$$R_{gd2} = \left(\frac{1}{g_{m1}} || r_{o1} \right) (1 + g_{m2}r_{o2}) + r_{o2}$$

And thus,

Assignment Project Exam Help

<https://powcoder.com>

C_L : Capacitor C_L sees the resistance between D_2 and ground which is r_{o2} ,

Add WeChat powcoder

Summing τ_{gd1} , τ_{gs1} , τ_{gs2} and τ_{CL} gives τ_H in the problem statement.

For the given numerical values:

$$A_M = -\frac{20}{1 + 20} (1 \times 20) = -19$$

$$\tau_{gd1} = C_{gd1} R_{sig} = 5 \times 20 = 100 \text{ ps}$$

$$\tau_{gs1} = C_{gs1} \frac{R_{sig} + r_{o1}}{1 + g_{m1}r_{o1}} = 20 \frac{20 + 20}{1 + 1 \times 20} = 38 \text{ ps}$$

$$\tau_{gd2} = C_{gd2} \left[\left(\frac{1}{g_{m1}} || r_{o1} \right) (1 + g_{m2}r_{o2}) + r_{o2} \right] = 5 [(1 || 20) (1+20) + 20] = 200 \text{ ps}$$

$$\tau_{CL} = C_L r_{o2} = 10 \times 20 = 200 \text{ ps}$$

$$\tau_H = 100 + 38 + 19 + 200 + 200 = 557 \text{ ps}$$

$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 557 \times 10^{-12}} = 286 \text{ MHz}$$

$$GB = 19 \times 286 = 5.43 \text{ GHz}$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder