

“In the name of God”

Tutorial of ECE 340 Course

Instructor: Professor Karim

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Seyyed Mojtaba Pourjaafari

Winter 2020

4.1 Figure 1 shows a discrete-circuit amplifier. The input signal v_{sig} is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite). All capacitors behave as short circuits for signals and as open circuits for dc.

(a) If the transistor has $V_t = 1V$, and $k_n = 4\text{ mA/V}^2$, verify that the bias circuit establishes $V_{GS} = 1.5\text{ V}$, $I_D = 0.5\text{ mA}$, and $V_D = +7\text{ V}$. That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.

(b) Find g_m and r_o if $V_A = 100\text{ V}$.

(c) Draw a complete small-signal equivalent circuit for the amplifier, assuming all capacitors behave as short circuits at signal frequencies.

(d) Find R_{in} , $\frac{v_{gs}}{v_{sig}}$, $\frac{v_o}{v_{gs}}$, and $\frac{v_o}{v_{sig}}$.

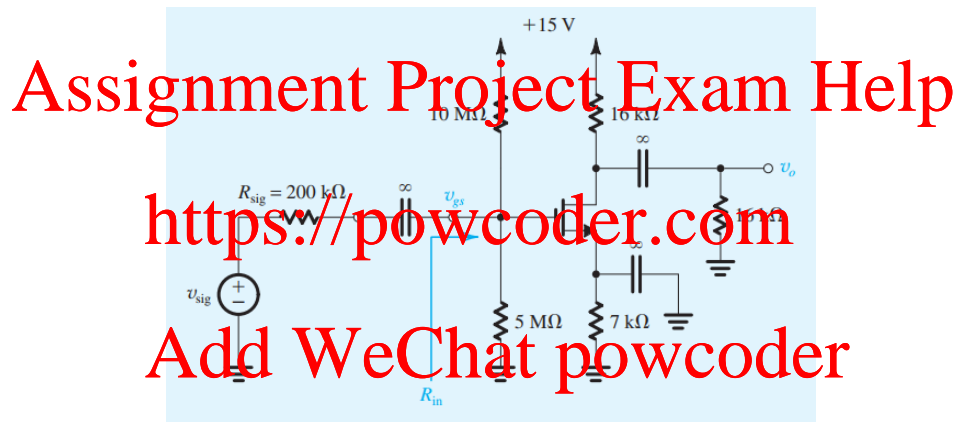


Figure 1

4.2 The NMOS transistor in the CS amplifier shown in Figure 2 has $V_t = 0.7\text{ V}$ and $V_A = 50\text{ V}$.

(a) Neglecting the Early effect, verify that the MOSFET is operating in saturation with $I_D = 0.5\text{ mA}$ and $V_{OV} = 0.3\text{ V}$. What must the MOSFET's k_n be? What is the dc voltage at the drain?

(b) Find R_{in} and G_v .

(c) If v_{sig} is a sinusoid with a peak amplitude $\widehat{v_{sig}}$, find the maximum allowable value of $\widehat{v_{sig}}$ for which the transistor remains in saturation. What is the corresponding amplitude of the output voltage?

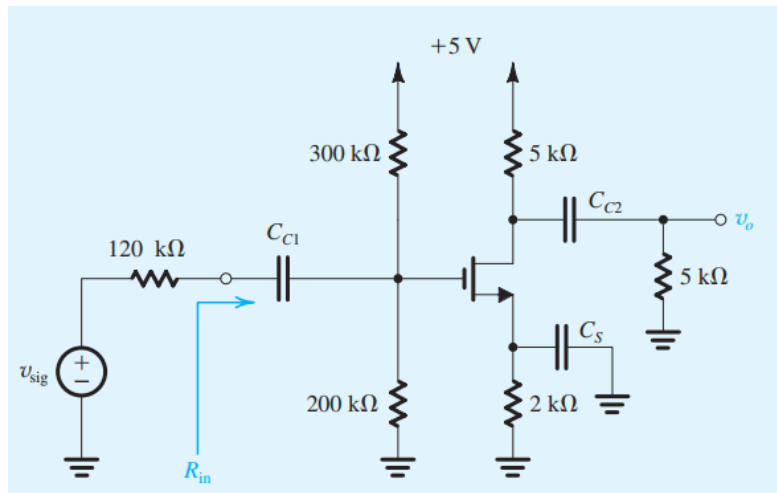


Figure 2

4.3 The MOSFET in the circuit of Figure 3 has $V_t = 0.8\text{ V}$, $k_n = 5 \frac{\text{mA}}{\text{V}^2}$ and $V_A = 40\text{ V}$.

- (a) Find the values of R_S , R_D and R_G so that $I_D = 0.4\text{ mA}$, the largest possible value for R_D is used while a maximum signal swing at the drain of $\pm 0.8\text{ V}$ is possible, and the input resistance at the gate is $10\text{ M}\Omega$.
- (b) Find the values of g_m and r_o at the bias point.
- (c) If terminal Z is grounded, terminal X is connected to a signal source having a resistance of $1\text{ M}\Omega$, and terminal Y is connected to a load resistance of $10\text{ k}\Omega$, find the voltage gain from signal source to load.
- (d) If terminal Y is grounded, find the voltage gain from X to Z with Z open-circuited. What is the output resistance of the source follower?
- (e) if terminal X is grounded and terminal Z is connected to a current source delivering a signal current of $50\text{ }\mu\text{A}$ and having a resistance of $100\text{ k}\Omega$, find the voltage signal that can be measured at Y.

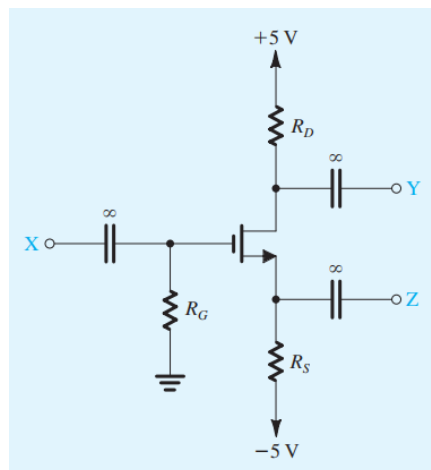


Figure 3