

“In the name of God”

Tutorial of ECE 340 Course

Instructor: Professor Karim

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

Seyyed Mojtaba Pourjaafari

Winter 2020

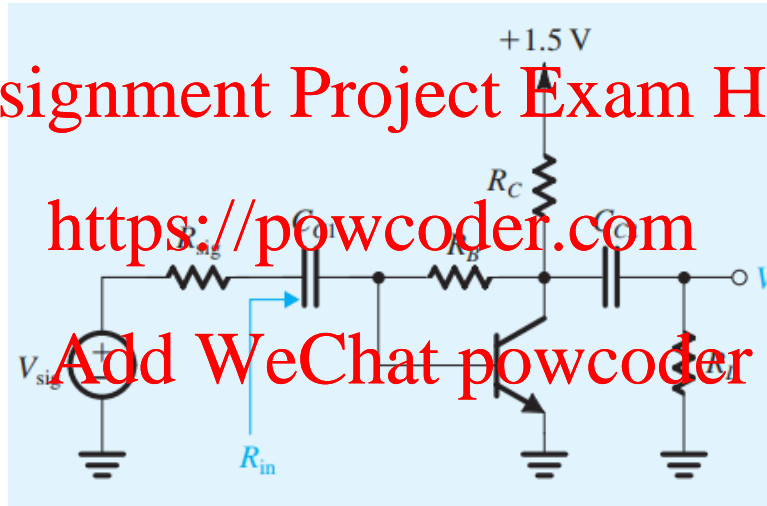5.1 The amplifier shown in Figure 1 has $R_{sig} = R_L = R_C = 1k\Omega$, $R_B = 47k\Omega$, $\beta = 100$, $C_\mu = 0.8 pF$, and $f_T = 600 MHz$. Assume the coupling capacitors to be very large.

- Find the dc collector current of the transistor.
- Find g_m and r_π .
- Neglecting r_o , find the midband voltage gain from base to collector
- Use the gain obtained in (c) to find the component of R_{in} that arises as a result of R_B . Hence find R_{in} .
- Find the overall gain at midband.
- Find C_{in} .
- Find f_H .




5.2 First consider the CS amplifier of Figure 2(a) show that $A_M = -g_m r_o$, $\tau_H = C_{gs} R_{sig} + C_{gd} [R_{sig} (1 + g_m r_o) + r_o] + C_L r_o$

Where C_L is the total capacitance between the output node and ground. Calculate the value of A_M , f_H and the gain-bandwidth product for the case $g_m = 1 \frac{mA}{V}$, $r_o = 20 k\Omega$, $R_{sig} = 20 k\Omega$, $C_{gs} = 20 fF$, $C_{gd} = 5 fF$, and $C_L = 10 fF$.

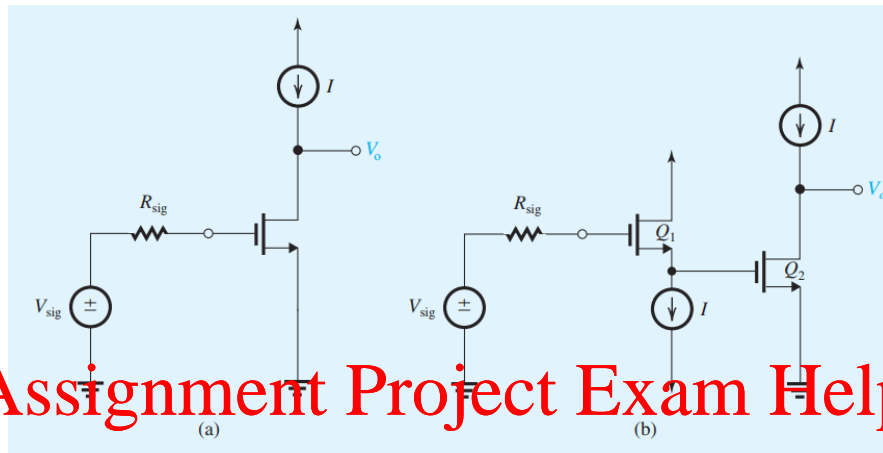(b) For the CD-CS amplifier in Figure 2(b), show that $A_M = -\frac{r_{o1}}{\frac{1}{g_{m1}} + r_{o1}} (g_{m2} r_{o2})$

$$\tau_H = C_{gd1}R_{sig} + C_{gs1}\frac{R_{sig} + r_{o1}}{1 + g_{m1}r_{o1}} + C_{gs2}\left(\frac{1}{g_{m1}} \parallel r_{o1}\right) + C_{gd2}\left[\left(\frac{1}{g_{m1}} \parallel r_{o1}\right)(1 + g_{m2}r_{o2}) + r_{o2}\right] + C_Lr_{o2}$$

Calculate the values of A_M , f_H , and the gain-bandwidth product for the same parameter values used in (a).



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder