

Name:

ID#:

ECE 340

Online Midterm Exam (1 hour 30 minutes)

Assignment Project Exam Help

February 25, 2021 (Winter 2021)

Answer all questions in the space provided (Open book exam)

Make reasonable assumptions as necessary.

Calculators are allowed.

30 minutes extra provided for online submission to the Learn Dropbox. Exams submitted after the 2 hour mark penalized at the rate of 1 mark per minute late.


NAME:

ID #:

Q1	/20
Q2	/20
Q3	/20
Total Mark:	/60

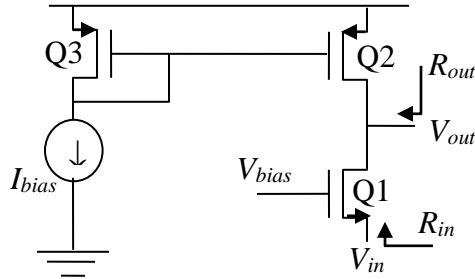1. Active Load Amplifier (20 marks)


For the circuit below, calculate the small signal R_{in} , R_{out} and gain V_{out}/V_{in} . (**5 marks each for total of 15 marks**) **Do not neglect r_o** . Identify at least two benefits the active load can provide? Based on the expressions derived for R_{in} and R_{out} , discuss at least three benefits/disadvantages that may arise from using the active load for the circuit shown below. (**5 marks**)



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

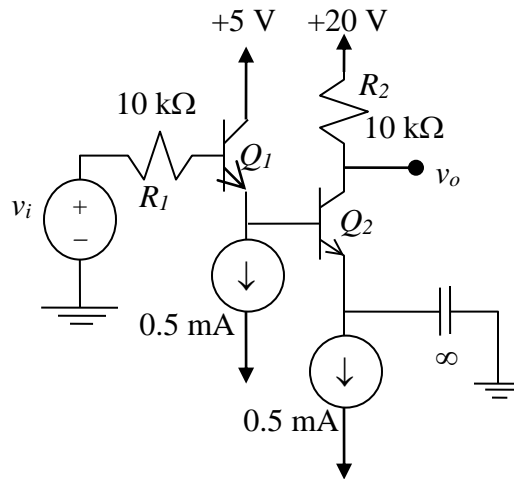2. Two-stage amplifiers and frequency response (20 marks)

For the circuit shown above, let $\beta = 100$, $C_\mu = 2$ pF, $f_T = 400$ MHz.

(a) Calculate the mid-band gain.

(10 marks)

<https://powcoder.com>

Add WeChat powcoder

Name:

ID#:

(b) Calculate the upper 3-dB frequency.

(10 marks)

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

3. Two-stage BiCMOS amplifier (20 marks)

A BiCMOS Darlington is shown in the figure below. The bias voltage V_B is adjusted for a dc output of 2 V. **Calculate** the bias currents in both devices (**5 marks each for a total of 10 marks**) and then **calculate** the small signal voltage gain v_o/v_i of the circuit. (**10 marks**)

For the MOS transistor, assume $W = 10\ \mu\text{m}$, $L = 1\ \mu\text{m}$, $\mu_n C_{OX} = 200\ \mu\text{A/V}^2$, $V_t = 0.6\ \text{V}$, $\gamma = 0.25\ \text{V}^{1/2}$, $\phi_f = 0.3\ \text{V}$ and $\lambda = 0$.

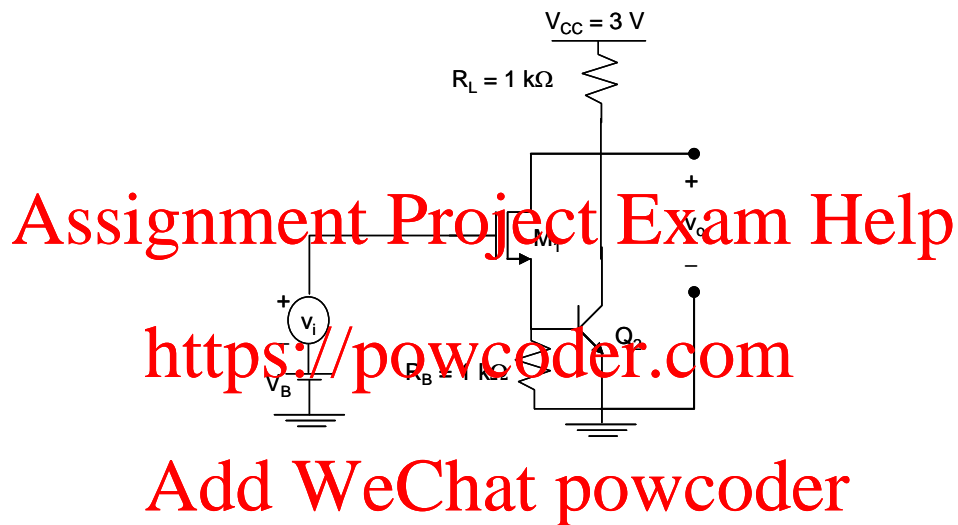For the BJT, assume $I_S = 10^{-16}\ \text{A}$, $\beta_F = 100$, $r_b = 0$, and $V_A \rightarrow \infty$.



Name:

ID#:

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder