

10.1 This problem deals with the series–shunt feedback amplifier of Fig. 1. The current-mirror loaded differential amplifier has a feedback network consisting of the voltage divider R_1 , R_2 , with $R_1 + R_2 = 1\text{ M}\Omega$. The devices are sized to operate at $|V_{OV}| = 0.2\text{ V}$. For all devices, $|V_A| = 10\text{ V}$. The input signal source has a zero-dc component.

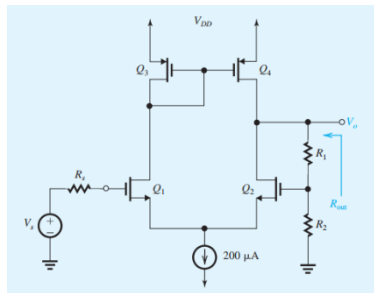


Figure 1

- Show that the feedback is negative.
- What do you expect the dc voltage at the gate of Q_2 to be? At the output? (Neglect the Early effect.)
- Find the A circuit. Derive an expression for A and find its value.
- Select values for R_1 and R_2 to obtain a closed-loop voltage gain $V_o/V_s = 5\text{ V/V}$.
- Find the value of R_{out} .
- Utilizing the open-circuit, closed-loop gain (5 V/V) and the value of R_{out} found in (e), find the value of gain obtained when a resistance $R_L = 10\text{ k}$ is connected to the output.
- As an alternative approach to (f) above, redo the analysis of the A circuit including R_L . Then utilize the values of R_1 and R_2 found in (d) to determine A_f . the value of A_f to that found in (f).

10.2

Figure 2 shows a three-stage feedback amplifier:

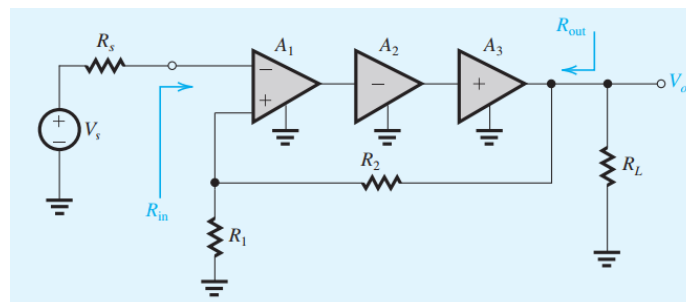


Figure 2

A1 has an $82\text{-k}\Omega$ differential input resistance, a 20-V/V open-circuit differential voltage gain, and a $3.2\text{-k}\Omega$ output resistance.

A2 has a $5\text{-k}\Omega$ input resistance, a 20-mA/V short-circuit transconductance, and a $20\text{-k}\Omega$ output resistance.

A3 has a $20\text{-k}\Omega$ input resistance, unity open-circuit voltage gain, and a $1\text{-k}\Omega$ output resistance. The feedback amplifier feeds a $1\text{-k}\Omega$ load resistance and is fed by a signal source with a $9\text{-k}\Omega$ resistance.

- (a) Show that the feedback is negative.
- (b) If $R_1 = 20\text{ k}\Omega$, find the value of R_2 that results in a closed-loop gain V_o/V_s that is ideally 5 V/V.
- (c) Supply the small-signal equivalent circuit.
- (d) Sketch the A circuit and determine A.
- (e) Find β and the amount of feedback.
- (f) Find the closed-loop gain $A_f \equiv V_o/V_s$.
- (g) Find the feedback amplifier's input resistance R_{in} .
- (h) Find the feedback amplifier's output resistance R_{out} .
- (i) If the high-frequency response of the open-loop gain A is dominated by a pole at 100 Hz, what is the upper 3-dB frequency of the closed-loop gain?
- (j) If for some reason A1 drops to half its nominal value, what is the percentage change in A_f ?