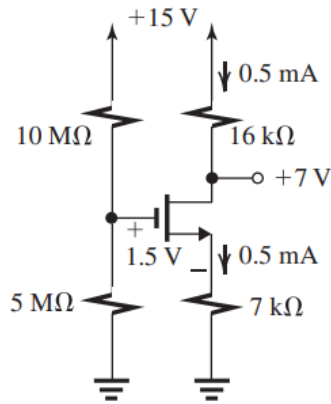


#### 4.1:

#### Solution

- (a) Open-circuit the capacitors to obtain the bias circuit shown in Figure 1, which indicates the given values.



From the voltage divider, we have  $V_G = 15 \times \frac{5}{10+5} = 5$  V

From the circuit, we obtain  $V_G = V_{GS} + 0.5 \times 7 = 1.5 + 3.5 = 5$  V. Which is consistent with the value provided by the voltage divider.

Since the drain voltage (+7 V) is higher than the gate voltage (+5 V), the transistor is operating in saturation.

From the circuit:

**Add WeChat powcoder**

$$V_D = V_{DD} - I_D R_D = 15 - 0.5 \times 16 = +7$$

$$V_{GS} = 1.5 \text{ V, thus } V_{OV} = 1.5 - V_t = 1.5 - 1 = 0.5 \text{ V}$$


$$I_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} \times 4 \times 0.5^2 = 0.5 \text{ mA}$$

(b)

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.5}{0.5} = 2 \frac{\text{mA}}{\text{V}}$$

$$r_o = \frac{V_A}{I_D} = \frac{100}{0.5} = 200 \text{ k}\Omega$$

(c)

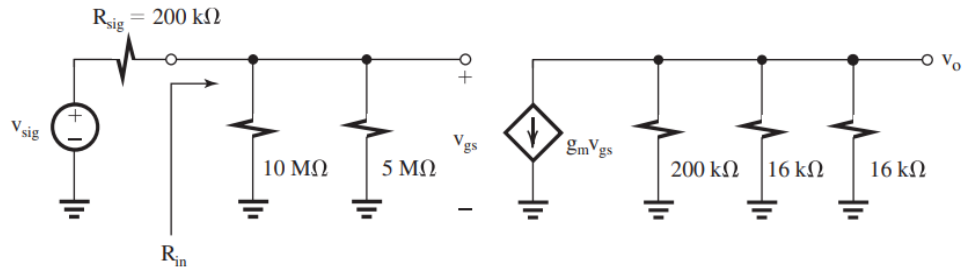

(d)

$$R_{in} = 10 \text{ M}\Omega || 5 \text{ M}\Omega = 3.33 \text{ M}\Omega$$

$$\frac{V_{gs}}{V_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{3.33}{3.33 + 0.2} = 0.94$$

$$\frac{V_o}{V_{gs}} = -g_m(200 || 16 || 16) = -2 \times 7.69 = -15.38$$

$$\frac{V_o}{V_{sig}} = \frac{V_{gs}}{V_{sig}} \times \frac{V_o}{V_{gs}} = -0.94 \times 15.38 = -14.5$$

Assignment Project Exam Help


4.2:

Solution

<https://powcoder.com>

(a) DC circuit is shown in Figure 2:

Add WeChat powcoder

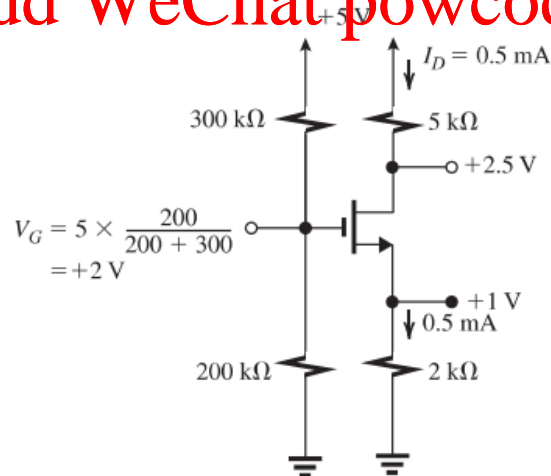

$$V_G = 2 \times I_D = 2 \times 0.5 = 1 \rightarrow V_{GS} = 2 - 1 = 1 \text{ V}$$


$$V_{OV} = V_{GS} - V_t = 1 - 0.7 = 0.3 \text{ V}$$

$V_D = 2.5 \text{ V}$  is higher than  $V_G - V_t = 1.3 \text{ V}$  by  $1.2 \text{ V}$ , so the circuit operating in saturation.

$$I_D = \frac{1}{2} k_n V_{OV}^2 \rightarrow 0.5 = \frac{1}{2} k_n \times 0.3^2 \rightarrow k_n = 11.1 \text{ mA/V}^2$$

(b)

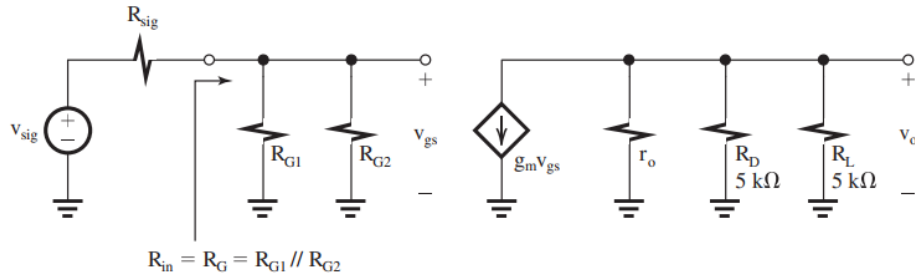The amplifier small-signal equivalent-circuit model is shown in figure 3:



$$R_{in} = R_{G1} || R_{G2} = 300 || 200 = 120 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.5}{0.3} = 3.33 \frac{\text{mA}}{\text{V}}$$

$$r_o = \frac{V_A}{I_D} = \frac{50}{0.5} = 100 \text{ k}\Omega$$

$$G_V = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (r_o || R_D || R_L) = -\frac{120}{120 + 120} \times 3.33 \times (100 || 5 || 5) = -4.1$$

(c)

$$V_G = 2 \text{ V}, \quad V_D = 2.5 \text{ V}$$

$$\widehat{V_{GS}} = 2 + \widehat{V_{gs}},$$

$$\widehat{V_{DS}} = 2.5 - |A_V| \widehat{V_{gs}}, \quad |A_V| = g_m (r_o || R_D || R_L) = 8.1$$

To remain in saturation,

$$\widehat{V_{DS}} \geq \widehat{V_{GS}} - V_t$$

$$2.5 - 8.1 \widehat{V_{gs}} \geq 2 + \widehat{V_{gs}} - 0.7 \quad \text{if we have equality: } \widehat{V_{gs}} = \frac{2.5 - 1.3}{9.1} = 0.132 \text{ V}$$

So, the corresponding value of  $\widehat{V_{gs}}$  is:

$$\widehat{V_{sig}} = \widehat{V_{gs}} \left( \frac{120 + 120}{120} \right) = 2 \times 0.132 = 0.264 \text{ V}. \text{ The corresponding amplitude at the output will be:}$$

$$|G_V| \widehat{V_{sig}} = 4.1 \times 0.264 = 1.08 \text{ V}$$

#### 4.3:

##### Solution:

(a) DC bias: When all capacitors eliminated:

$$R_{in} \text{ at gate} = R_G = 10 \text{ M}\Omega$$

$$V_G = 0, \text{ thus } V_S = -V_{GS}, \text{ where } V_{GS} \text{ can be obtained from: } I_D = \frac{1}{2} k_n V_{OV}^2 \rightarrow 0.4 = \frac{1}{2} \times 5 \times V_{OV}^2 \rightarrow$$

$$V_{OV} = 0.4 \text{ V} \rightarrow V_{GS} = V_t + 0.4 = 0.8 + 0.4 = 1.2 \text{ V}$$

$$V_S = -1.2 \text{ V}$$

$$R_S = \frac{-1.2 - (-5)}{0.4} = 9.5 \text{ k}\Omega$$

To remain in saturation, the minimum drain voltage must be limited to  $V_G - V_t = 0 - 0.8 = -0.8 \text{ V}$ .  
Now, to allow for 0.8 V negative signal swing, we must have:

$$V_D = 0 \text{ V}$$

$$R_D = \frac{5 - 0}{0.4} = 12.5 \text{ k}\Omega$$

(b)

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.4}{0.4} = 2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_D} = \frac{40}{0.4} = 100 \text{ k}\Omega$$

(c)

If terminal Z connected to ground. The circuit becomes a CS amplifier,


$$G_V = -\frac{V_y}{V_{sig}} = \frac{R_G}{R_G + R_{sig}} \times -g_m(r_o || R_D || R_L) = -\frac{10}{10 + 1} \times 2 \times (100 || 12.5 || 10) = -9.6$$

(d) If terminal Y is grounded, the circuit becomes a CD or source-follower amplifier:

$$\frac{V_Z}{V_x} = \frac{(R_S || r_o)}{(R_S || r_o) + \frac{1}{g_m}} = \frac{(9.5 || 100)}{(9.5 || 100) + \frac{1}{2}} = 0.946$$

$$\text{Looking into terminal Z, we see } R_o = R_S || r_o || \frac{1}{g_m} = 9.5 || 100 || \frac{1}{2} = 473 \Omega$$

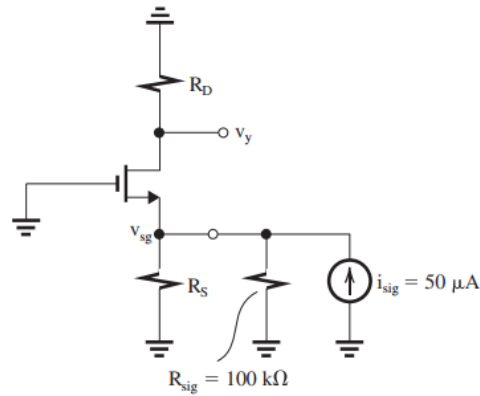(e) IF X is grounded, the circuit becomes a CG amplifier:



The figure shows the circuit prepared for signal calculations:

$$V_{sg} = i_{sig} \times \left[ R_{sig} || R_S || \frac{1}{g_m} \right] = 50 \times 10^{-3} \left[ 100 || 9.5 || \frac{1}{2} \right] = 0.024 \text{ V}$$

$$V_y = (g_m R_D) V_{sg} = (2 \times 12.5) \times 0.024 = 0.6 \text{ V}$$

# Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder