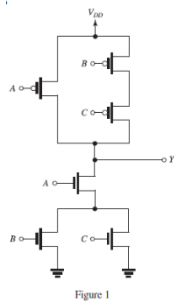


9.1

Solution:



The logic function realized can be written from the PDN as:


$$\bar{Y} = A(B + C) \text{ or equivalently:}$$

$$Y = \overline{A(B + C)}$$

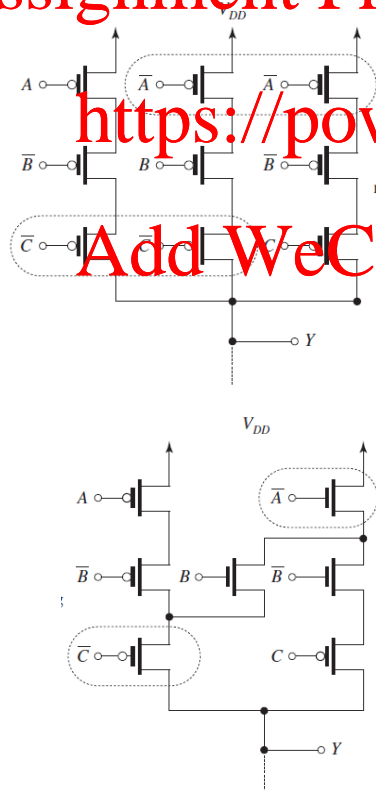9.2:

Solution:

Inspecting the PUN circuit reveal the potential for eliminating two transistors through what is known as path merging.



However, an alternative way to synthesize a PDN with a lower number of transistors. By using the DeMorgan's law:

$$\bar{Y} = \overline{ABC} \cdot \overline{ABC} \cdot \overline{ABC} = (A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


9.3:

Solution:

$$NM_H = V_{OH} - V_{IH} = 1.5 - 1.2 = 0.3 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 1.1 - 0.3 = 0.8 \text{ V}$$

b)

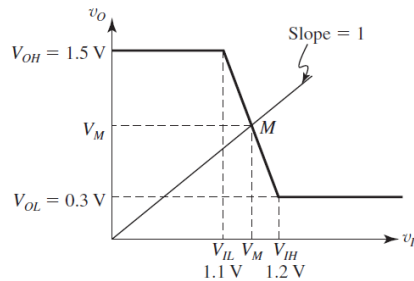

$$\text{Slope} = \frac{V_{OH} - V_{OL}}{V_{IL} - V_{IH}} = \frac{1.5 - 0.3}{1.1 - 1.2} = -12$$

Thus,

$$\frac{V_M - 0.3}{V_M - 1.2} = -12 \rightarrow V_M = 1.15 \text{ V}$$

Add WeChat powcoder

C) The voltage gain in the transition region is equal to the slope found above, thus Gain=-12