

### Exercise 6–1

**Ex: 6.1**  $i_C = I_S e^{v_{BE}/V_T}$

$$v_{BE2} - v_{BE1} = V_T \ln \left[ \frac{i_{C2}}{i_{C1}} \right]$$

$$v_{BE2} = 700 + 25 \ln \left[ \frac{0.1}{1} \right]$$

$$= 642 \text{ mV}$$

$$v_{BE3} = 700 + 25 \ln \left[ \frac{10}{1} \right]$$

$$= 758 \text{ mV}$$

**Ex: 6.2**  $\therefore \alpha = \frac{\beta}{\beta + 1}$

$$\frac{50}{50+1} < \alpha < \frac{150}{150+1}$$

$$0.980 < \alpha < 0.993$$

**Ex: 6.3**  $I_C = I_E - I_B$

$$= 1.460 \text{ mA} - 0.01446 \text{ mA}$$

$$= 1.446 \text{ mA}$$

**Assignment Project Exam Help**  
 $v_{BE} = 690 \text{ mV}$

$$\alpha = \frac{I_C}{I_E} = \frac{1.446}{1.460} = 0.979$$

$$\beta = \frac{I_C}{I_B} = \frac{1.446}{0.01446} = 100$$

$$I_C = I_S e^{v_{BE}/V_T}$$

$$I_S = \frac{I_C}{e^{v_{BE}/V_T}} = \frac{1.446}{e^{700/25}}$$

$$= \frac{1.446}{e^{28}} \text{ mA} = 10^{-15} \text{ A}$$

**Ex: 6.4**  $\beta = \frac{\alpha}{1 - \alpha}$  and  $I_C = 10 \text{ mA}$

$$\text{For } \alpha = 0.99, \beta = \frac{0.99}{1 - 0.99} = 99$$

$$I_B = \frac{I_C}{\beta} = \frac{10}{99} = 0.1 \text{ mA}$$

$$\text{For } \alpha = 0.98, \beta = \frac{0.98}{1 - 0.98} = 49$$

$$I_B = \frac{I_C}{\beta} = \frac{10}{49} = 0.2 \text{ mA}$$

**Ex: 6.5** Given:

$$I_S = 10^{-16} \text{ A}, \beta = 100, I_C = 1 \text{ mA}$$

We write

$$I_{SE} = I_{SC}/\alpha = I_S = \left(1 + \frac{1}{\beta}\right)$$

$$= 10^{-16} \times 1.01 = 1.01 \times 10^{-16} \text{ A}$$


$$I_{SB} = \frac{I_S}{\beta} = \frac{10^{-16}}{100} = 10^{-18} \text{ A}$$

$$V_{BE} = V_T \ln \left[ \frac{I_C}{I_S} \right] = 25 \ln \left[ \frac{1 \text{ mA}}{10^{-16}} \right]$$

$$= 25 \times 29.9336$$

$$= 748 \text{ mV}$$

**Ex: 6.6**

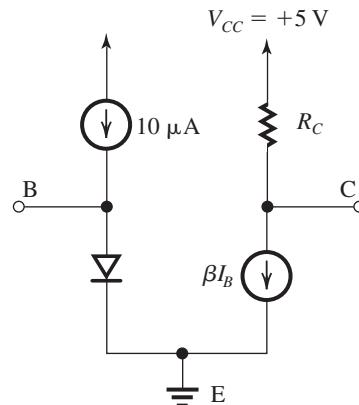

$$I_C = 1 \text{ mA}$$

For active range  $V_C \geq V_B$ ,

$$R_{C\max} = \frac{V_{CC} - 0.690}{I_C}$$

$$= \frac{5 - 0.69}{1} = 4.31 \text{ kΩ}$$

**Ex: 6.7**  $I_S = 10^{-15} \text{ A}$

$$\text{Area}_C = 100 \times \text{Area}_E$$

$$I_{SC} = 100 \times I_S = 10^{-13} \text{ A}$$

**Ex: 6.8**  $i_C = I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}$

for  $i_C = 0$

$$I_S e^{v_{BE}/V_T} = I_{SC} e^{v_{BC}/V_T}$$

$$\frac{I_{SC}}{I_S} = \frac{e^{v_{BE}/V_T}}{e^{v_{BC}/V_T}}$$

$$= e^{(v_{BE} - v_{BC})/V_T}$$

$$\therefore V_{CE} = V_{BE} - V_{BC} = V_T \ln \left[ \frac{I_{SC}}{I_S} \right]$$

For collector Area = 100 × Emitter area

$$V_{CE} = 25 \ln \left[ \frac{100}{1} \right] = 115 \text{ mV}$$

Exercise 6-2

**Ex: 6.9**  $I_C = I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}$

$$I_B = \frac{I_S}{\beta} e^{v_{BE}/V_T} + I_{SC} e^{v_{BC}/V_T}$$

$$\beta_{\text{forced}} = \left. \frac{I_C}{I_B} \right|_{\text{sat}} < \beta$$

$$= \beta \frac{I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}}{I_S e^{v_{BE}/V_T} + \beta I_{SC} e^{v_{BC}/V_T}}$$


$$= \beta \frac{I_S e^{(v_{BE}-v_{BC})/V_T} - I_{SC}}{I_S e^{(v_{BE}-v_{BC})/V_T} + \beta I_{SC}}$$

$$= \beta \frac{e^{V_{CE\text{sat}}/V_T} - I_{SC}/I_S}{e^{V_{CE\text{sat}}/V_T} + \beta I_{SC}/I_S} \quad \text{Q.E.D.}$$

$$\beta_{\text{forced}} = 100 \frac{e^{200/25} - 100}{e^{200/25} + 100 \times 100}$$

$$= 100 \times 0.2219 \approx 22.2$$

**Ex: 6.10**

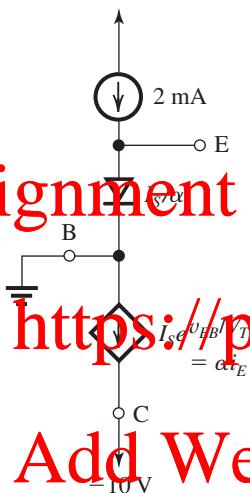

# Assignment Project Exam Help

<https://powcoder.com>  
Add WeChat powcoder

$$I_E = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$$

$$2 \text{ mA} = \frac{51}{50} 10^{-14} e^{v_{BE}/V_T}$$

$$V_{BE} = 25 \ln \left[ \frac{2}{10^3} \times \frac{50}{51} \times 10^{14} \right]$$

$$= 650 \text{ mV}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = \frac{50}{51} \times 2$$

$$= 1.96 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{1.96}{50} \Rightarrow 39.2 \mu\text{A}$$


**Ex: 6.11**  $I_C = I_S e^{v_{BE}/V_T} = 1.5 \text{ A}$

$$\therefore V_{BE} = V_T \ln [1.5/10^{-11}]$$

$$= 25 \times 25.734$$

$$= 643 \text{ mV}$$

**Ex: 6.12**

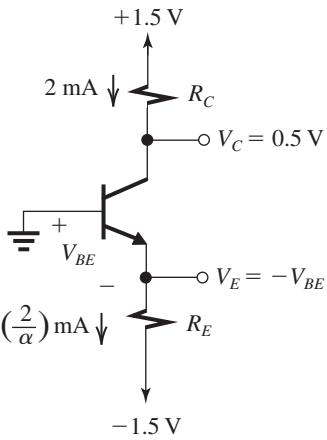

$$R_C = \frac{1.5 - V_C}{I_C} = \frac{1.5 - 0.5}{2} = 0.5 \text{ k}\Omega = 500 \Omega$$

Since at  $I_C = 1 \text{ mA}$ ,  $V_{BE} = 0.8 \text{ V}$ , then at  $I_C = 2 \text{ mA}$ ,

$$V_{BE} = 0.8 + 0.025 \ln \left( \frac{2}{0.8} \right) = 0.8 + 0.017 = 0.817 \text{ V}$$

$$V_E = -V_{BE} = -0.817 \text{ V}$$

$$I_E = \frac{2 \text{ mA}}{\alpha} = \frac{2}{0.99} = 2.02 \text{ mA}$$


$$I_E = \frac{V_E - (-1.5)}{R_E}$$

Thus,

$$R_E = \frac{-0.817 + 1.5}{2.02} = 0.338 \text{ k}\Omega$$

$$= 338 \Omega$$

**Ex: 6.13**

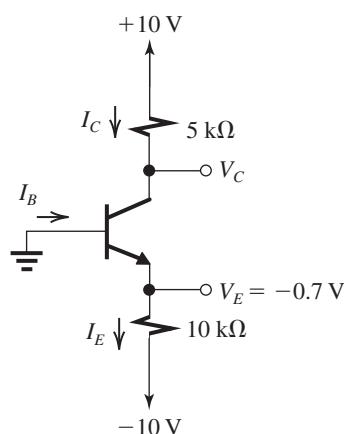

### Exercise 6-3

$$I_E = \frac{V_E - (-10)}{10} = \frac{-0.7 + 10}{10}$$

$$= 0.93 \text{ mA}$$

Assuming active-mode operation,

$$I_B = \frac{I_E}{\beta + 1} = \frac{0.93}{50 + 1} = 0.0182 \text{ mA}$$

$$= 18.2 \mu\text{A}$$


$$I_C = I_E - I_B = 0.93 - 0.0182 = 0.91 \text{ mA}$$

$$V_C = 10 - I_C \times 5$$

$$= 10 - 0.91 \times 5 = 5.45 \text{ V}$$

Since  $V_C > V_B$ , the transistor is operating in the active mode, as assumed.

### Ex: 6.14

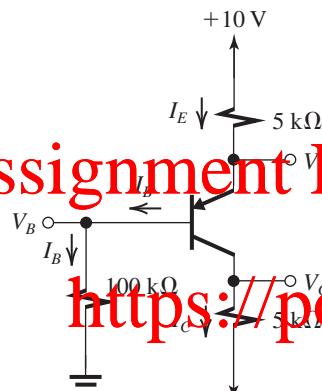

## Assignment Project Exam Help

<https://powcoder.com>  
Add WeChat powcoder

$$V_B = 1.0 \text{ V}$$

Thus,

$$I_B = \frac{V_B}{100 \text{ k}\Omega} = 0.01 \text{ mA}$$

$$V_E = +1.7 \text{ V}$$

Thus,

$$I_E = \frac{10 - V_E}{5 \text{ k}\Omega} = \frac{10 - 1.7}{5} = 1.66 \text{ mA}$$

and

$$\beta + 1 = \frac{I_E}{I_B} = \frac{1.66}{0.01} = 166$$

$$\Rightarrow \beta = 165$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{165}{165 + 1} = 0.994$$

Assuming active-mode operation,


$$I_C = \alpha I_E = 0.994 \times 1.66 = 1.65 \text{ mA}$$

and

$$V_C = -10 + 1.65 \times 5 = -1.75 \text{ V}$$

Since  $V_C < V_B$ , the transistor is indeed operating in the active mode.

### Ex: 6.15

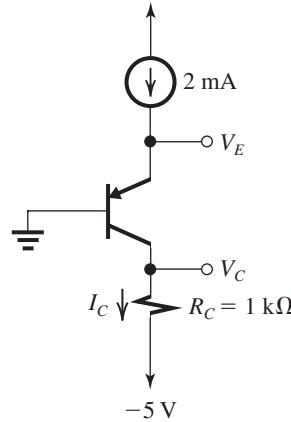

The transistor is operating at a constant emitter current. Thus, a change in temperature of  $+30^\circ\text{C}$  results in a change in  $V_E$  by

$$\Delta V_{EB} = -2 \text{ mV} \times 30 = -60 \text{ mV}$$

Thus,

$$\Delta V_E = -60 \text{ mV}$$

Since the collector current remains unchanged at  $\alpha I_E$ , the collector voltage does not change:

$$\Delta V_C = 0 \text{ V}$$

### Ex: 6.16 Refer to Fig. 6.19(a):

$$i_C = I_S e^{v_{BE}/V_T} + \frac{v_{CE}}{r_o} \quad (1)$$

Now using Eqs. (6.21) and (6.22), we can express  $r_o$  as

$$r_o = \frac{V_A}{I_S e^{v_{BE}/V_T}}$$

Substituting in Eq. (1), we have

$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

which is Eq. (6.18). Q.E.D.

$$\text{Ex: 6.17 } r_o = \frac{V_A}{I_C} = \frac{100}{I_C}$$

At  $I_C = 0.1 \text{ mA}$ ,  $r_o = 1 \text{ M}\Omega$

At  $I_C = 1 \text{ mA}$ ,  $r_o = 100 \text{ k}\Omega$

At  $I_C = 10 \text{ mA}$ ,  $r_o = 10 \text{ k}\Omega$

### Exercise 6-4

**Ex: 6.18**  $\Delta I_C = \frac{\Delta V_{CE}}{r_o}$


where

$$r_o = \frac{V_A}{I_C} = \frac{100}{1} = 100 \text{ k}\Omega$$

$$\Delta I_C = \frac{11 - 1}{100} = 0.1 \text{ mA}$$

Thus,  $I_C$  becomes 1.1 mA.

**Ex: 6.19**

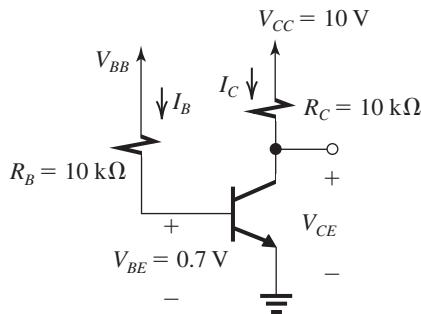

## Assignment Project Exam Help

(a) For operation in the active mode with  $V_{CE} = 5 \text{ V}$ ,

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{10 - 5}{10} = 0.5 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.5}{50} = 0.01 \text{ mA}$$

$$V_{BB} = V_{BE} + I_B R_B \\ = 0.7 + 0.01 \times 10 = 0.8 \text{ V}$$

(b) For operation at the edge of saturation,

$$V_{CE} = 0.3 \text{ V}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 0.3}{10} = 0.97 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.97}{50} = 0.0194 \text{ mA}$$

$$V_{BB} = V_B + I_B R_B$$

$$= 0.7 + 0.0194 \times 10 = 0.894 \text{ V}$$

(c) For operation deep in saturation with  $\beta_{\text{forced}} = 10$ , we have

$$V_{CE} \simeq 0.2 \text{ V}$$

$$I_C = \frac{10 - 0.2}{10} = 0.98 \text{ mA}$$

$$I_B = \frac{I_C}{\beta_{\text{forced}}} = \frac{0.98}{10} = 0.098 \text{ mA}$$

$$V_{BB} = V_B + I_B R_B$$

$$= 0.7 + 0.098 \times 10 = 1.68 \text{ V}$$

**Ex: 6.20** For  $V_{BB} = 0 \text{ V}$ ,  $I_B = 0$  and the transistor is cut off. Thus,

$$I_C = 0$$

and

$$V_C = V_{CC} = +10 \text{ V}$$

**Ex: 6.21** Refer to the circuit in Fig. 6.22 and let  $V_{BB} = 1.7 \text{ V}$ . The current  $I_B$  can be found from

$$I_B = \frac{V_{BB} - V_B}{R_B} = \frac{1.7 - 0.7}{10} = 0.1 \text{ mA}$$

Assuming operation in the active mode,

$$I_C = \beta I_B = 50 \times 0.1 = 5 \text{ mA}$$

Thus,

$$V_C = V_{CC} - R_C I_C$$

$$= 10 - 1 \times 5 = 5 \text{ V}$$

which is greater than  $V_B$ , verifying that the transistor is operating in the active mode, as assumed.

(a) To obtain operation at the edge of saturation,  $R_C$  must be increased to the value that results in  $V_{CE} = 0.3 \text{ V}$ :

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} \\ = \frac{10 - 0.3}{0.97} = 1.94 \text{ k}\Omega$$

(b) Further increasing  $R_C$  results in the transistor operating in saturation. To obtain saturation-mode operation with  $V_{CE} = 0.2 \text{ V}$  and  $\beta_{\text{forced}} = 10$ , we use

$$I_C = \beta_{\text{forced}} \times I_B \\ = 10 \times 0.1 = 1 \text{ mA}$$

The value of  $R_C$  required can be found from

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} \\ = \frac{10 - 0.2}{1} = 9.8 \text{ k}\Omega$$

**Ex: 6.22** Refer to the circuit in Fig. 6.23(a) with the base voltage raised from 4 V to  $V_B$ . If at this value of  $V_B$ , the transistor is at the edge of saturation then,

$$V_C = V_B - 0.4 \text{ V}$$

Since  $I_C \simeq I_E$ , we can write


$$\frac{10 - V_C}{R_C} = \frac{V_E}{R_E} = \frac{V_B - 0.7}{R_E}$$

Thus,

$$\frac{10 - (V_B - 0.4)}{4.7} = \frac{V_B - 0.7}{3.3}$$

$$\Rightarrow V_B = +4.7 \text{ V}$$

**Ex: 6.23**

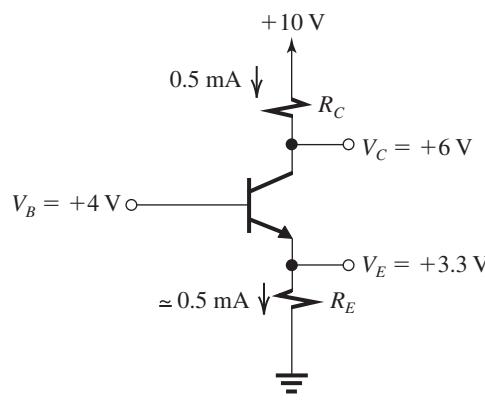

To establish a reverse-bias voltage of 2 V across the CBJ,  
 $V_C = +6 \text{ V}$

From the figure we see that


$$R_C = \frac{10 - 6}{0.5} = 8 \text{ k}\Omega$$

and

$$R_E = \frac{3.3}{0.5} = 6.6 \text{ k}\Omega$$

where we have assumed  $\alpha \approx 1$ .

**Ex: 6.24**

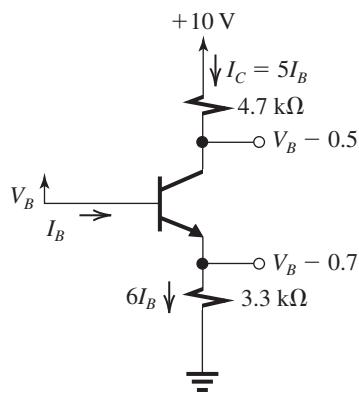

The figure shows the circuit with the base voltage at  $V_B$  and the BJT operating in saturation with  $V_{CE} = 0.2 \text{ V}$  and  $\beta_{\text{forced}} = 5$ .

$$I_C = 5I_B = \frac{10 - (V_B - 0.5)}{4.7} \quad (1)$$

$$I_E = 6I_B = \frac{V_B - 0.7}{3.3} \quad (2)$$

Dividing Eq. (1) by Eq. (2), we have

$$\frac{5}{6} = \frac{10.5 - V_B}{V_B - 0.7} \times \frac{3.3}{4.7}$$

$$\Rightarrow V_B = +5.18 \text{ V}$$

**Ex: 6.25** Refer to the circuit in Fig. 6.26(a). The largest value for  $R_C$  while the BJT remains in the active mode corresponds to

$$V_C = +0.4 \text{ V}$$

Since the emitter and collector currents remain unchanged, then from Fig. 6.26(b) we obtain


$$I_C = 4.6 \text{ mA}$$

Thus,

$$R_C = \frac{V_C - (-10)}{I_C}$$

$$= \frac{+0.4 + 10}{4.6} = 2.26 \text{ k}\Omega$$

**Ex: 6.26**

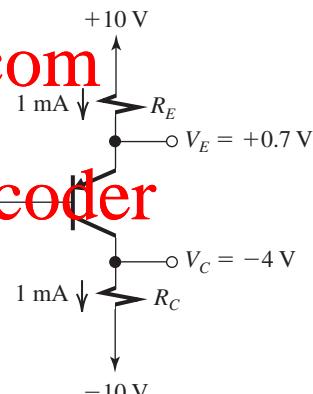

For a 4-V reverse-biased voltage across the CBJ,

$$V_C = -4 \text{ V}$$

Refer to the figure.

$$I_C = 1 \text{ mA} = \frac{V_C - (-10)}{R_C}$$

$$\Rightarrow R_C = \frac{-4 + 10}{1} = 6 \text{ k}\Omega$$

$$R_E = \frac{10 - V_E}{I_E}$$

Assuming  $\alpha = 1$ ,

$$R_E = \frac{10 - 0.7}{1} = 9.3 \text{ k}\Omega$$

**Ex: 6.27** Refer to the circuit in Fig. 6.27:

$$I_B = \frac{5 - 0.7}{100} = 0.043 \text{ mA}$$

To ensure that the transistor remains in the active mode for  $\beta$  in the range 50 to 150, we need to select  $R_C$  so that for the highest collector current possible, the BJT reaches the edge of saturation, that is,  $V_{CE} = 0.3 \text{ V}$ . Thus,

$$V_{CE} = 0.3 = 10 - R_C I_{C\max}$$

where

$$I_{C\max} = \beta_{\max} I_B$$

$$= 150 \times 0.043 = 6.45 \text{ mA}$$

Thus,

$$R_C = \frac{10 - 0.3}{6.45} = 1.5 \text{ k}\Omega$$

For the lowest  $\beta$ ,

$$I_C = \beta_{\min} I_B$$

$$= 50 \times 0.043 = 2.15 \text{ mA}$$

and the corresponding  $V_{CE}$  is

$$V_{CE} = 10 - R_C I_C = 10 - 1.5 \times 2.15$$

$$= 6.775 \text{ V}$$

Thus,  $V_{CE}$  will range from 0.3 V to 6.8 V.

**Add WeChat powcoder**

**Ex: 6.28** Refer to the solution of Example 6.10.

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + [R_{BB}/(\beta + 1)]}$$

$$= \frac{5 - 0.7}{3 + (33.3/51)} = 1.177 \text{ mA}$$

$$I_C = \alpha I_E = 0.98 \times 1.177 = 1.15 \text{ mA}$$

Thus the current is reduced by

$$\Delta I_C = 1.28 - 1.15 = 0.13 \text{ mA}$$

which is a -10% change.


**Ex: 6.29** Refer to the circuit in Fig. 6.30(b). The total current drawn from the power supply is

$$I = 0.103 + 1.252 + 2.78 = 4.135 \text{ mA}$$

Thus, the power dissipated in the circuit is

$$P = 15 \text{ V} \times 4.135 \text{ mA} = 62 \text{ mW}$$

**Ex: 6.30**

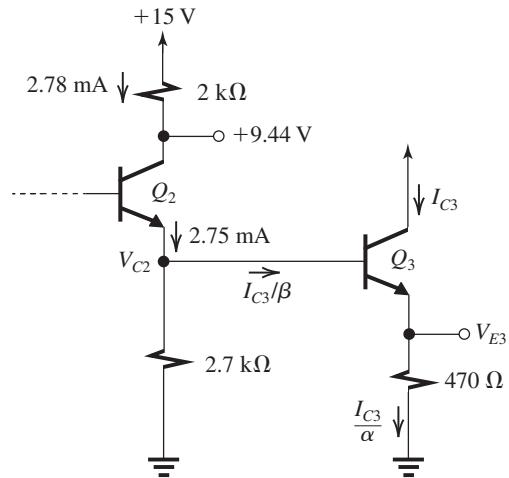

From the figure we see that

$$V_{E3} = \frac{I_{C3}}{\alpha} \times 0.47$$

$$V_{C2} = V_{E3} + 0.7 = \frac{I_{C3}}{\alpha} \times 0.47 + 0.7 \quad (1)$$

A node analysis at the collector of  $Q_2$  yields

$$2.75 = \frac{V_{C2}}{2.7} + \frac{I_{C3}}{\beta}$$

Substituting for  $V_{C2}$  from Eq. (1), we obtain

$$2.75 = \frac{(0.47 I_{C3}/\alpha) + 0.7}{2.7} + \frac{I_{C3}}{\beta}$$

Substituting  $\alpha = 0.99$  and  $\beta = 100$  and solving for  $I_{C3}$  results in


$$I_{C3} = 13.4 \text{ mA}$$

Now,  $V_{E3}$  and  $V_{C2}$  can be determined:

$$V_{E3} = \frac{I_{C3}}{\alpha} \times 0.47 = \frac{13.4}{0.99} \times 0.47 = +6.36 \text{ V}$$

$$V_{C2} = V_{E3} + 0.7 = +7.06 \text{ V}$$

**Ex: 6.31**

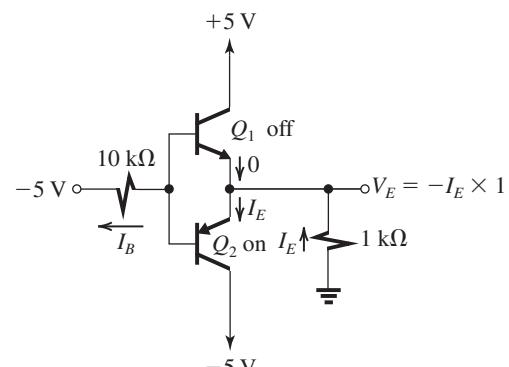

### Exercise 6-7

From the figure we see that  $Q_1$  will be off and  $Q_2$  will be on. Since the base of  $Q_2$  will be at a voltage higher than  $-5$  V, transistor  $Q_2$  will be operating in the active mode. We can write a loop equation for the loop containing the  $10\text{-k}\Omega$  resistor, the EBJ of  $Q_2$  and the  $1\text{-k}\Omega$  resistor:

$$-I_E \times 1 - 0.7 - I_B \times 10 = -5$$

Substituting  $I_B = I_E/(\beta + 1) = I_E/101$  and rearranging gives

$$I_E = \frac{5 - 0.7}{\frac{10}{101} + 1} = 3.9 \text{ mA}$$

Thus,

$$V_E = -3.9 \text{ V}$$

$$V_{B2} = -4.6 \text{ V}$$

$$I_B = 0.039 \text{ mA}$$

**Ex: 6.32** With the input at  $+10$  V, there is a strong possibility that the conducting transistor

$Q_1$  will be saturated. Assuming this to be the case, the analysis steps will be as follows:

$$V_{CEsat}|_{Q_1} = 0.2 \text{ V}$$

$$V_E = 5 \text{ V} - V_{CEsat} = +4.8 \text{ V}$$

$$I_{E1} = \frac{4.8 \text{ V}}{1 \text{ k}\Omega} = 4.8 \text{ mA}$$

$$V_{B1} = V_E + V_{BE1} = 4.8 + 0.7 = +5.5 \text{ V}$$

$$I_{B1} = \frac{10 - 5.5}{10} = 0.45 \text{ mA}$$

$$I_{C1} = I_{E1} - I_{B1} = 4.8 - 0.45 = 4.35 \text{ mA}$$

$$\beta_{forced} = \frac{I_C}{I_B} = \frac{4.35}{0.45} = 9.7$$

which is lower than  $\beta_{min}$ , verifying that  $Q_1$  is indeed saturated.

Finally, since  $Q_2$  is off,


$$I_{C2} = 0$$

**Ex: 6.33**  $V_O = +10 - BV_{BCO} = 10 - 70$

$$= -60 \text{ V}$$

## Assignment Project Exam Help

This figure belongs to Exercise 6.32

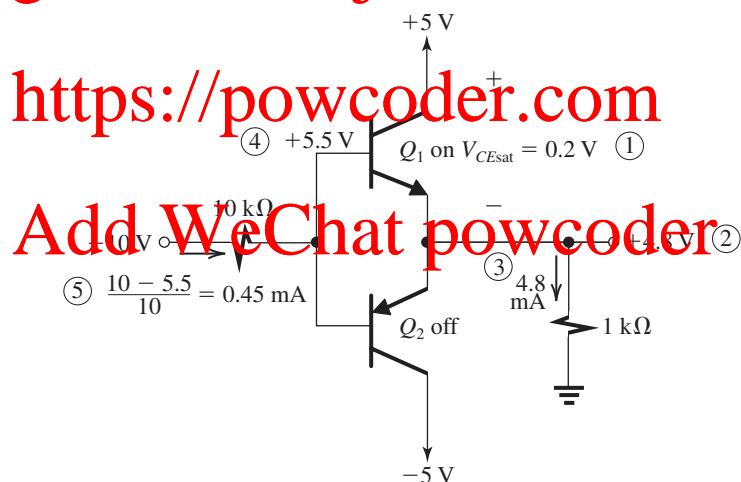

- 6.1**
1. Active
  2. Saturation
  3. Active
  4. Saturation
  5. Active
  6. Cutoff

**6.2** The EB junctions have a 4:1 area ratio.

$$I_C = I_S e^{V_{BE}/V_T}$$

$$0.5 \times 10^{-3} = I_{S1} \times e^{0.75/0.025}$$

$$\Rightarrow I_{S1} = 4.7 \times 10^{-17} \text{ A}$$

$$I_{S2} = 4I_{S1} = 1.87 \times 10^{-16} \text{ A}$$

**6.3**  $I_C = I_S e^{V_{BE}/V_T}$

$$200 \times 10^{-6} = I_S e^{30}$$

$$\Rightarrow I_S = 1.87 \times 10^{-17} \text{ A}$$

For the transistor that is 32 times larger,

$$I_S = 32 \times 1.87 \times 10^{-17}$$

$$= 6 \times 10^{-16} \text{ A}$$

At  $V_{BE} = 30 \text{ V}_T$ , the larger transistor conducts a current of

$$I_C = 32 \times 200 \mu\text{A} = 0.4 \text{ mA}$$

At  $I_C = 1 \text{ mA}$ , the base-emitter voltage of the larger transistor can be found as

$$1 \times 10^{-3} = 6 \times 10^{-16} e^{V_{BE}/V_T}$$

$$V_{BE} = V_T \ln\left(\frac{1 \times 10^{-3}}{6 \times 10^{-16}}\right) = 0.704 \text{ V}$$

**6.4**  $\frac{I_{S1}}{I_{S2}} = \frac{A_{E1}}{A_{E2}} = \frac{200 \times 200}{0.4 \times 0.4} = 250,000$

$$I_{C1} = I_{S1} e^{V_{BE1}/V_T}$$

$$I_{C2} = I_{S2} e^{V_{BE2}/V_T}$$

For  $I_{C1} = I_{C2}$  we have

$$e^{(V_{BE2}-V_{BE1})/V_T} = \frac{I_{S1}}{I_{S2}} = 250,000$$

$$V_{BE2} - V_{BE1} = 0.025 \ln(250,000)$$

$$= 0.31 \text{ V}$$

**6.5**  $I_{C1} = 10^{-13} e^{700/25} = 0.145 \text{ A} = 145 \text{ mA}$

$$I_{C2} = 10^{-18} e^{700/25} = 1.45 \mu\text{A}$$

For the first transistor 1 to conduct a current of  $1.45 \mu\text{A}$ , its  $V_{BE}$  must be

$$V_{BE1} = 0.025 \ln\left(\frac{1.45 \times 10^{-6}}{10^{-13}}\right)$$

$$= 0.412 \text{ V}$$

**6.6** Old technology:

$$10^{-3} = 2 \times 10^{-15} e^{V_{BE}/V_T}$$

$$V_{BE} = 0.025 \ln\left(\frac{10^{-3}}{2 \times 10^{-15}}\right) = 0.673 \text{ V}$$

New technology:

$$10^{-3} = 2 \times 10^{-18} e^{V_{BE}/V_T}$$

$$V_{BE} = 0.025 \ln\left(\frac{10^{-3}}{2 \times 10^{-18}}\right) = 0.846 \text{ V}$$

**6.7**  $5 \times 10^{-3} = I_S e^{0.76/0.025}$  (1)

$$I_C = I_S e^{0.70/0.025}$$
 (2)

Dividing Eq. (2) by Eq. (1) yields

$$I_C = 5 \times 10^{-3} e^{-0.06/0.025}$$

$$= 0.45 \text{ mA}$$

For  $I_C = 5 \mu\text{A}$ ,

$$5 \times 10^{-6} = I_S e^{V_{BE}/0.025}$$
 (3)

Dividing Eq. (3) by Eq. (1) yields

$$10^{-3} = e^{(V_{BE}-0.76)/0.025}$$

$$V_{BE} = 0.76 + 0.025 \ln(10^{-3})$$

$$= 0.587 \text{ V}$$

**6.8**  $I_B = 10 \mu\text{A}$

$$I_C = 800 \mu\text{A}$$

$$\beta = \frac{I_C}{I_B} = 80$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{80}{81} = 0.988$$

**6.9**

$\alpha$	0.5	0.8	0.9	0.95	0.98	0.99	0.995	0.999
$\beta = \frac{\alpha}{1-\alpha}$	1	4	9	19	49	99	199	999

**6.10**

$\beta$	1	2	10	20	50	100	200	500	1000
$\alpha = \frac{\beta}{\beta + 1}$	0.5	0.67	0.91	0.95	0.98	0.99	0.995	0.998	0.999

**6.11**  $\beta = \frac{\alpha}{1-\alpha}$  (1)

$$\alpha \rightarrow \alpha + \Delta\alpha$$

$$\beta \rightarrow \beta + \Delta\beta$$

$$\beta + \Delta\beta = \frac{\alpha + \Delta\alpha}{1-\alpha - \Delta\alpha}$$
 (2)

Subtracting Eq. (1) from Eq. (2) gives

$$\begin{aligned}\Delta\beta &= \frac{\alpha + \Delta\alpha}{1 - \alpha - \Delta\alpha} - \frac{\alpha}{1 - \alpha} \\ \Delta\beta &= \frac{\Delta\alpha}{(1 - \alpha - \Delta\alpha)(1 - \alpha)}\end{aligned}\quad (3)$$

Dividing Eq. (3) by Eq. (1) gives

$$\frac{\Delta\beta}{\beta} = \left(\frac{\Delta\alpha}{\alpha}\right) \left(\frac{1}{1 - \alpha - \Delta\alpha}\right)$$

For  $\Delta\alpha \ll 1$ , the second factor on the right-hand side is approximately equal to  $\beta$ . Thus

$$\frac{\Delta\beta}{\beta} \simeq \beta \left(\frac{\Delta\alpha}{\alpha}\right) \quad \text{Q.E.D.}$$

For  $\frac{\Delta\beta}{\beta} = -10\%$  and  $\beta = 100$ ,

$$\frac{\Delta\alpha}{\alpha} \simeq \frac{-10\%}{100} = -0.1\%$$

**6.12** Transistor is operating in active region:

$$\beta = 50 \rightarrow 300$$

## Assignment Project Exam Help

$$I_B = 10 \mu\text{A}$$

$$I_C = \beta I_B = 0.5 \text{ mA} \rightarrow 3 \text{ mA}$$

$$I_E = (\beta + 1)I_B = 0.51 \text{ mA} \rightarrow 3.01 \text{ mA}$$

Maximum power dissipated in transistor is

$$I_B \times 0.7 \text{ V} + I_C \times V_C$$

$$= 0.01 \times 0.7 + 3 \times 10 \simeq 30 \text{ mW}$$

## Add WeChat powcoder

$$\text{6.13 } i_C = I_S e^{v_{BE}/V_T}$$

$$= 5 \times 10^{-15} e^{0.7/0.025} = 7.2 \text{ mA}$$

$i_B$  will be in the range  $\frac{7.2}{50}$  mA to  $\frac{7.2}{200}$  mA, that is, 144  $\mu\text{A}$  to 36  $\mu\text{A}$ .

$i_E$  will be in the range  $(7.2 + 0.144)$  mA to  $(7.2 + 0.036)$  mA, that is, 7.344 mA to 7.236 mA.

**6.14** For  $i_B = 10 \mu\text{A}$ ,

$$i_C = i_E - i_B = 1000 - 10 = 990 \mu\text{A}$$

$$\beta = \frac{i_C}{i_B} = \frac{990}{10} = 99$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{99}{100} = 0.99$$

For  $i_B = 20 \mu\text{A}$ ,

$$i_C = i_E - i_B = 1000 - 20 = 980 \mu\text{A}$$

$$\beta = \frac{i_C}{i_B} = \frac{980}{20} = 49$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{49}{50} = 0.98$$

For  $i_B = 50 \mu\text{A}$ ,

$$i_C = i_E - i_B = 1000 - 50 = 950 \mu\text{A}$$

$$\beta = \frac{i_C}{i_B} = \frac{950}{50} = 19$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{19}{20} = 0.95$$

**6.15** See Table below.

**6.16** First we determine  $I_S$ ,  $\beta$ , and  $\alpha$ :

$$1 \times 10^{-3} = I_S e^{700/25}$$

$$= I_S \cdot 6.91 \times 10^{-16} \text{ A}$$

$$\beta = \frac{I_C}{I_B} = \frac{1 \text{ mA}}{10 \mu\text{A}} = 100$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99$$

Then we can determine  $I_{SE}$  and  $I_{SB}$ :




$$I_{SE} = \frac{I_S}{\alpha} = 6.98 \times 10^{-16} \text{ A}$$

$$I_{SB} = \frac{I_S}{\beta} = 6.91 \times 10^{-18} \text{ A}$$

The figure on next page shows the four large-signal models, corresponding to Fig. 6.5(a) to (d), together with their parameter values.

This table belongs to Problem 6.15.

Transistor	a	b	c	d	e
$V_{BE}$ (mV)	700	690	580	780	820
$I_C$ (mA)	1.000	1.000	0.230	10.10	73.95
$I_B$ ( $\mu\text{A}$ )	10	20	5	120	1050
$I_E$ (mA)	1.010	1.020	0.235	10.22	75
$\alpha$	0.99	0.98	0.979	0.988	0.986
$\beta$	100	50	46	84	70
$I_S$ (A)	$6.9 \times 10^{-16}$	$1.0 \times 10^{-15}$	$1.9 \times 10^{-14}$	$2.8 \times 10^{-16}$	$4.2 \times 10^{-16}$

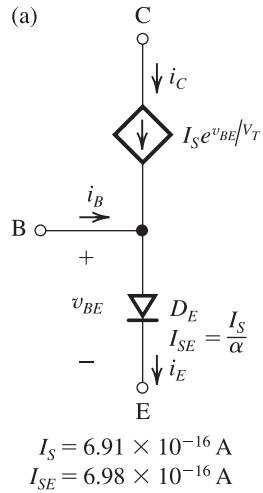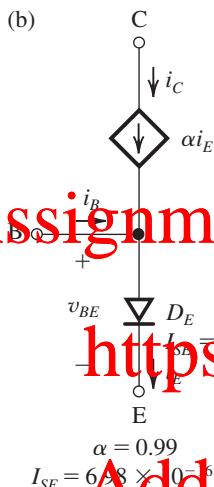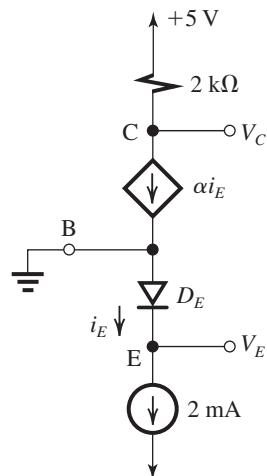**6.17**

The figure shows the circuit, where

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99$$

$$I_{SE} = \frac{I_S}{\alpha} = \frac{5 \times 10^{-15}}{0.99} = 5.05 \times 100^{-15} \text{ A}$$

The voltage at the emitter  $V_E$  is

$$V_E = -V_{DE}$$

$$= -V_T \ln(I_E/I_{SE})$$

$$\geq -0.025 \ln\left(\frac{2 \times 10^{-3}}{5.05 \times 10^{-15}}\right)$$

$$= -0.668 \text{ V}$$

The voltage at the collector  $V_C$  is found from

$$V_C = 5 - I_C \times 2$$

$$= 5 - \alpha I_E \times 2$$

$$= 5 - 0.99 \times 2 \times 2 = 1.04 \text{ V}$$

**6.18** Refer to the circuit in Fig. 6.6(b).

$$I_{SB} = \frac{I_S}{\beta} = \frac{5 \times 10^{-15}}{50} = 10^{-16} \text{ A}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.5 \times 10^{-3}}{50} = 10^{-5} \text{ A}$$

$$V_B = V_{BE} = V_T \ln\left(\frac{I_B}{I_{SB}}\right)$$



$$= 0.025 \ln\left(\frac{10^{-5}}{10^{-16}}\right)$$

$$= 0.633 \text{ V}$$

We can determine  $R_B$  from

$$R_B = \frac{V_{CC} - V_B}{I_B}$$

$$= \frac{15 - 0.633}{10^{-5}} = 1.44 \text{ M}\Omega$$

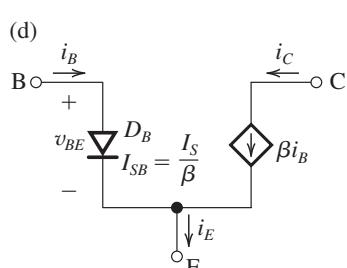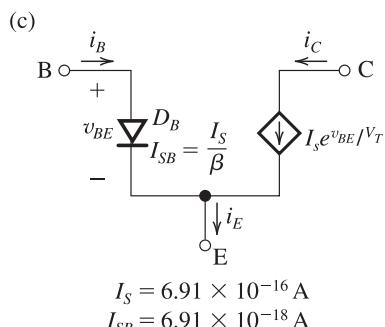**Assignment Project Exam Help**<https://powcoder.com>**Add WeChat powcoder**

To obtain  $V_{CE} = 1$  V, we select  $R_C$  according to

$$\begin{aligned} R_C &= \frac{V_{CC} - V_{CE}}{I_C} \\ &= \frac{15 - 1}{0.5} = 28 \text{ k}\Omega \end{aligned}$$

**6.19**  $I_S = 10^{-15}$  A

Thus, a forward-biased EBJ conducting a current of 1 mA will have a forward voltage drop  $V_{BE}$ :

$$\begin{aligned} V_{BE} &= V_T \ln\left(\frac{I}{I_S}\right) \\ &= 0.025 \ln\left(\frac{10^{-3}}{10^{-15}}\right) = 0.691 \text{ V} \end{aligned}$$

$$I_{SC} = 100I_S = 10^{-13} \text{ A}$$

Thus, a forward-biased CBJ conducting a 1-mA current will have a forward voltage drop  $V_{BC}$ :

$$V_{BC} = V_T \ln\left(\frac{1 \times 10^{-3}}{1 \times 10^{-13}}\right) = 0.576 \text{ V}$$

When forward-biased with 0.5 V, the emitter-base junction conducts

$$I = I_S e^{0.5/0.025}$$

$$= 10^{-15} e^{0.5/0.025} = 0.47 \mu\text{A}$$

and the CBJ conducts

$$I = I_{SC} e^{0.5/0.025}$$

$$= 10^{-13} e^{0.5/0.025} = 48.5 \mu\text{A}$$

**6.20** The equations utilized are

$$v_{BC} = v_{BE} - v_{CE} = 0.7 - v_{CE}$$

$$i_{BC} = I_{SC} e^{v_{BC}/V_T} = 10^{-13} e^{v_{BC}/0.025}$$

$$i_{BE} = I_{SB} e^{v_{BE}/V_T} = 10^{-17} e^{0.7/0.025}$$

$$i_B = i_{BC} + i_{BE}$$

$$i_C = I_S e^{v_{BE}/V_T} - i_{BC} = 10^{-15} e^{0.7/0.025} - i_{BC}$$

Performing these calculations for  $v_{CE} = 0.4$  V, 0.3 V, and 0.2 V, we obtain the results shown in the table below.

This table belongs to Problem 6.20.

$v_{CE}$ (V)	$v_{BC}$ (V)	$i_{BC}$ ( $\mu\text{A}$ )	$i_{BE}$ ( $\mu\text{A}$ )	$i_B$ ( $\mu\text{A}$ )	$i_C$ ( $\text{mA}$ )	$i_C/i_B$
0.4	0.3	0.016	14.46	14.48	1.446	100
0.3	0.4	0.89	14.46	15.35	1.445	94
0.2	0.5	48.5	14.46	62.96	1.398	29

**6.21** Dividing Eq. (6.14) by Eq. (6.15) and substituting  $i_C/i_B = \beta_{\text{forced}}$  gives

$$\beta_{\text{forced}} = \frac{I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T}}{(I_S/\beta) e^{v_{BE}/V_T} + I_{SC} e^{v_{BC}/V_T}}$$

Dividing the numerator and denominator of the right-hand side by  $I_{SC} e^{v_{BC}/V_T}$  and replacing  $v_{BE} - v_{BC}$  by  $V_{CE\text{sat}}$  gives

$$\beta_{\text{forced}} = \frac{\left(\frac{I_S}{I_{SC}}\right) e^{V_{CE\text{sat}}/V_T} - 1}{\frac{1}{\beta} \left(\frac{I_S}{I_{SC}}\right) e^{V_{CE\text{sat}}/V_T} + 1}$$

This equation can be used to obtain  $e^{V_{CE\text{sat}}/V_T}$  and hence  $V_{CE\text{sat}}$  as


$$\left(\frac{I_S}{I_{SC}}\right) e^{V_{CE\text{sat}}/V_T} = \frac{1 + \beta_{\text{forced}}}{1 - \beta_{\text{forced}}/\beta}$$

$$\Rightarrow V_{CE\text{sat}} = V_T \ln \left[ \frac{I_{SC}}{I_S} \frac{1 + \beta_{\text{forced}}}{1 - \beta_{\text{forced}}/\beta} \right] \quad \text{Q.E.D.}$$

For  $\beta = 100$  and  $I_{SC}/I_S = 100$ , we can use this equation to obtain  $V_{CE\text{sat}}$  corresponding to the given values of  $\beta_{\text{forced}}$ . The results are as follows:

$\beta_{\text{forced}}$	50	10	5	1
$V_{CE\text{sat}}$ (V)	0.261	0.178	0.161	0.133

## 6.22

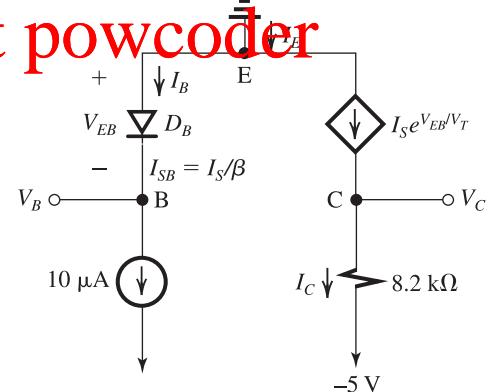

The emitter-base voltage  $V_{EB}$  is found as the voltage drop across the diode  $D_B$ , whose scale

current is  $I_{SB} = I_S/\beta$ , it is conducting a  $10\text{-}\mu\text{A}$  current. Thus,

$$V_{EB} = V_T \ln\left(\frac{10 \mu\text{A}}{I_{SB}}\right)$$

where

$$I_{SB} = \frac{I_S}{\beta} = \frac{10^{-14}}{50} = 2 \times 10^{-16} \text{ A}$$

$$V_{EB} = 0.025 \ln\left(\frac{10 \times 10^{-6}}{2 \times 10^{-16}}\right)$$

$$= 0.616 \text{ V}$$

Thus,

$$V_B = -V_{EB} = -0.616 \text{ V}$$

The collector current can be found as

$$I_C = \beta I_B$$

$$= 50 \times 10 = 500 \mu\text{A} = 0.5 \text{ mA}$$

The collector voltage can now be obtained from

$$V_C = -5 + I_C \times 8.2 = -5 + 0.5 \times 8.2 = -0.9 \text{ V}$$

The emitter current can be found as

$$I_E = I_B + I_C = 10 + 500 = 510 \mu\text{A}$$

$$= 0.51 \text{ mA}$$

**6.23** At  $i_C = 1 \text{ mA}$ ,  $v_{EB} = 0.7 \text{ V}$

At  $i_C = 10 \text{ mA}$ ,

$$v_{EB} = 0.7 + V_T \ln\left(\frac{10}{1}\right)$$

$$= 0.7 + 0.025 \ln(10) = 0.758 \text{ V}$$


At  $i_C = 100 \text{ mA}$ ,

$$v_{EB} = 0.7 + 0.025 \ln\left(\frac{100}{1}\right)$$

$$= 0.815 \text{ V}$$

Note that  $v_{EB}$  increases by about 60 mV for every decade increase in  $i_C$ .

**6.24**

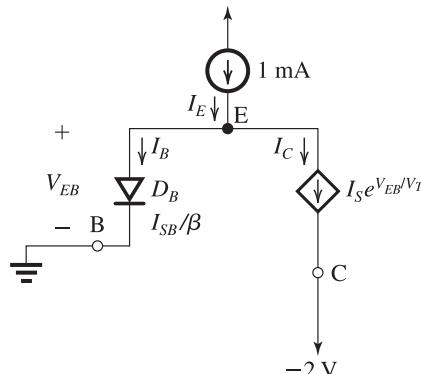

Referring to the figure, we see that

$$I_E = I_B + I_C = \frac{I_C}{\beta} + I_C$$

Thus,

$$I_C = \frac{I_E}{1 + \frac{1}{\beta}} = \frac{1}{1 + \frac{1}{10}} = 0.909 \text{ mA}$$

$$I_B = 0.091 \text{ mA}$$

For direction of flow, refer to the figure.

$$V_{EB} = V_T \ln\left(\frac{I_B}{I_{SB}}\right)$$

where

$$I_{SB} = \frac{I_S}{\beta} = \frac{10^{-15}}{10} = 10^{-16} \text{ A}$$

$$V_{EB} = 0.025 \ln\left(\frac{0.091 \times 10^{-3}}{10^{-16}}\right)$$

$$= 0.688 \text{ V}$$

Thus,

$$V_C = V_B - V_{EB} = -1.088 - 0.688 \text{ V}$$

If a transistor with  $\beta = 1000$  is substituted,

$$I_C = \frac{I_E}{1 + \frac{1}{\beta}} = \frac{1}{1 + \frac{1}{1000}} = 0.999 \text{ mA}$$

Thus,  $I_C$  changes by  $0.999 - 0.909 = 0.09 \text{ mA}$ , a 9.9% increase.

**6.25** Add WeChat powcoder

$$I_B = \frac{I_E}{\beta + 1} = \frac{5}{20 + 1} = 0.238 \text{ A} = 238 \text{ mA}$$

$$I_C = I_S e^{V_{EB}/V_T}$$

$$\alpha I_E = I_S e^{V_{EB}/V_T}$$

where

$$\alpha = \frac{20}{21} = 0.95$$

$$I_S = \alpha I_E e^{-V_{EB}/V_T}$$

$$= 0.95 \times 5 e^{-(0.8/0.025)}$$

$$= 6 \times 10^{-14} \text{ A}$$


A transistor that conducts  $I_C = 1 \text{ mA}$  with  $V_{EB} = 0.70 \text{ V}$  has a scale current

$$I_S = 1 \times 10^{-3} e^{-0.70/0.025} = 6.9 \times 10^{-16} \text{ A}$$


The emitter-base junction areas of these two transistors will have the same ratio as that of their scale currents, thus

$$\frac{\text{EBJ area of first transistor}}{\text{EBJ area of second transistor}} = \frac{6 \times 10^{-14}}{6.9 \times 10^{-16}} = 87$$

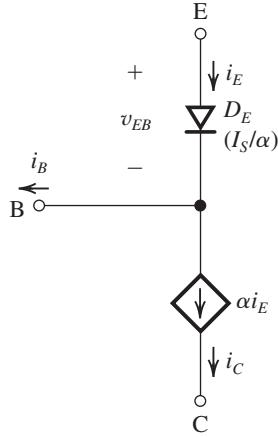**6.26** The two missing large-signal equivalent circuits for the *pnp* transistor are those corresponding to the *npn* equivalent circuits in Fig. 6.5(b) and 6.5(d). They are shown in the figure.




# Assignment Project Exam Help

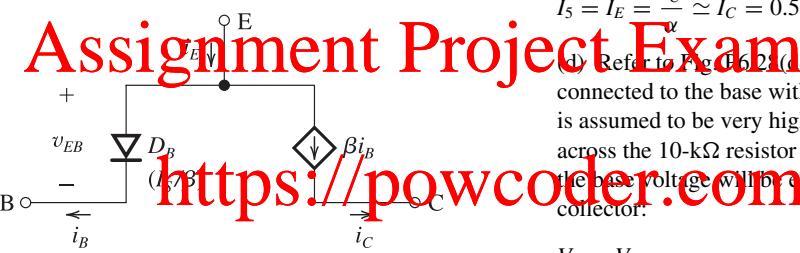

**6.27**

# Add WeChat powcoder

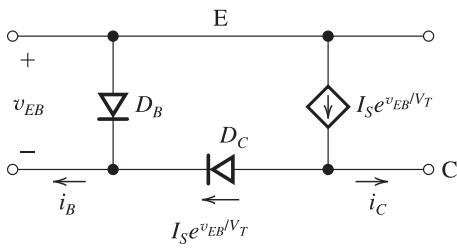

**6.28** (a) Refer to Fig. P6.28(a).

$$I_1 = \frac{10.7 - 0.7}{5 \text{ k}\Omega} = 2 \text{ mA}$$

Assuming operation in the active mode,

$$I_C = \alpha I_1 \simeq I_1 = 2 \text{ mA}$$

$$V_2 = -10.7 + I_C \times 5$$

$$= -10.7 + 2 \times 5 = -0.7 \text{ V}$$

Since  $V_2$  is lower than  $V_B$ , which is 0 V, the transistor is operating in the active mode, as assumed.

(b) Refer to Fig. P6.28(b).

Since  $V_C = -4 \text{ V}$  is lower than  $V_B = -2.7 \text{ V}$ , the transistor is operating in the active mode.

$$I_C = \frac{-4 - (-10)}{2.4 \text{ k}\Omega} = 2.5 \text{ mA}$$

$$I_E = \frac{I_C}{\alpha} \simeq I_C = 2.5 \text{ mA}$$

$$V_3 = +12 - I_E \times 5.6 = 12 - 2.5 \times 5.6 = -2 \text{ V}$$

(c) Refer to Fig. P6.28(c) and use

$$I_C = \frac{0 - (-10)}{20} = 0.5 \text{ mA}$$

Assuming active-mode operation, and utilizing the fact that  $\beta$  is large,  $I_B \simeq 0$  and

$$V_4 \simeq 2 \text{ V}$$

Since  $V_C < V_B$ , the transistor is indeed operating in the active region.

$$I_S = I_E = \frac{I_C}{\alpha} \simeq I_C = 0.5 \text{ mA}$$

(d) Refer to Fig. P6.28(d). Since the collector is connected to the base with a 10-kΩ resistor and  $\beta$  is assumed to be very high, the voltage drop across the 10-kΩ resistor will be close to zero and the base voltage will be equal to that of the collector:

$$V_B = V_7$$

This also implies active-mode operation. Now,

$$V_E = V_B - 0.7$$

Thus,

$$V_E = V_7 - 0.7$$

$$\begin{aligned} I_6 &= \frac{V_E - (-10)}{3} \\ &= \frac{V_7 - 0.7 + 10}{3} = \frac{V_7 + 9.3}{3} \end{aligned} \quad (1)$$

Since  $I_B = 0$ , the collector current will be equal to the current through the 9.1-kΩ resistor,

$$I_C = \frac{+10 - V_7}{9.1} \quad (2)$$


Since  $\alpha \simeq 1$ ,  $I_C = I_E = I_6$  resulting in

$$\frac{10 - V_7}{9.1} = \frac{V_7 + 9.3}{3}$$

$$\Rightarrow V_7 = -4.5 \text{ V}$$

and

$$I_6 = \frac{V_7 + 9.3}{3} = \frac{-4.5 + 9.3}{3} = 1.6 \text{ mA}$$

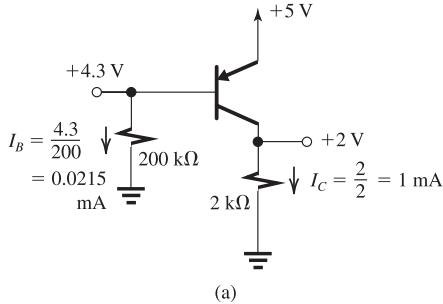**6.29 (a)**

(a)

Since  $V_C$  is lower than  $V_B$ , the transistor is operating in the active region. From the figure corresponding to Fig. P6.29(a), we see that

$$I_C = 1 \text{ mA}$$


$$I_B = 0.0215 \text{ mA}$$

Thus,

$$\beta \equiv \frac{I_C}{I_B} = \frac{1}{0.0215} = 46.5$$

(b)

# Assignment Project Exam Help

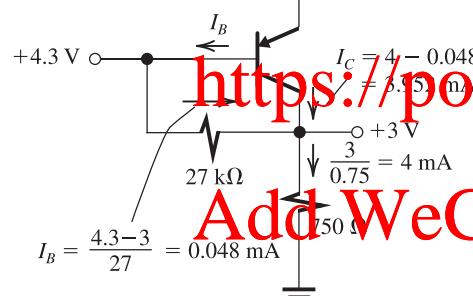


(b)

Observe that with  $V_C$  at 3 V and  $V_B$  at 4.3 V, the transistor is operating in the active region. Refer to the analysis shown in the figure, which leads to

$$\beta \equiv \frac{I_C}{I_B} = \frac{3.952}{0.048} = 82.3$$

(c)

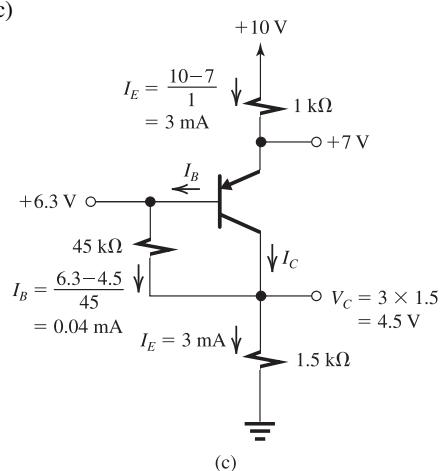


Observe that the transistor is operating in the active region and note the analysis performed on the circuit diagram. Thus,

$$I_C = I_E - I_B = 3 - 0.04 = 2.96 \text{ mA}$$

and

$$\beta \equiv \frac{I_C}{I_B} = \frac{2.96}{0.04} = 74$$

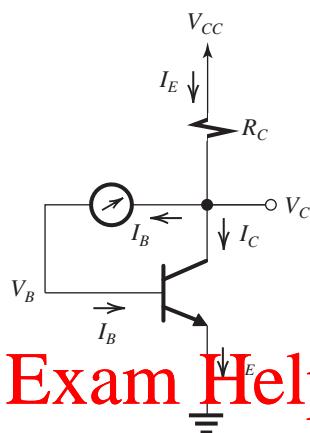**6.30**

Since the meter resistance is small,  $V_C \approx V_B$  and the transistor is operating in the active region. To obtain  $I_E = 1$  mA, we arrange that  $V_{BE} = 0.7$  V. Since  $V_C \approx V_B$ ,  $V_C$  must be set to 0.7 by selecting  $R_C$  according to

$$V_C = 0.7 = V_{CC} - I_E R_C$$

Thus,

$$0.7 = 9 - 1 \times R_C$$

$$\Rightarrow R_C = 8.3 \text{ k}\Omega$$

Since the meter reads full scale when the current flowing through it (in this case,  $I_B$  is 50 μA), a full-scale reading corresponds to


$$\beta \equiv \frac{I_C}{I_B} \approx \frac{1 \text{ mA}}{50 \mu\text{A}} = 20$$

If the meter reads 1/5 of full scale, then  $I_B = 10 \mu\text{A}$  and

$$\beta = \frac{1 \text{ mA}}{10 \mu\text{A}} = 100$$

A meter reading of 1/10 full scale indicates that

$$\beta = \frac{1 \text{ mA}}{5 \mu\text{A}} = 200$$

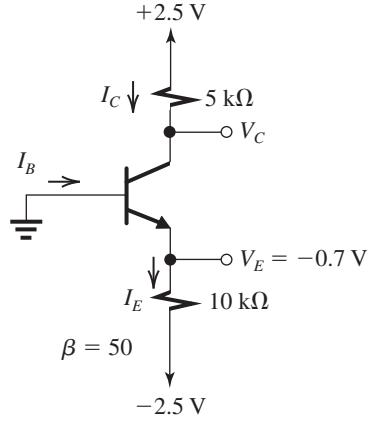**6.31**

$$I_E = \frac{V_E - (-2.5)}{10} = \frac{-0.7 + 2.5}{10} = 0.18 \text{ mA}$$


Assuming the transistor is operating in the active mode, we obtain

$$I_B = \frac{I_E}{\beta + 1} = \frac{0.18}{50 + 1} = 3.6 \mu\text{A}$$

$$I_C = \left( \frac{\beta}{\beta + 1} \right) I_E = \frac{50}{51} \times 0.18 = 0.176 \text{ mA}$$

$$V_C = +2.5 - I_C R_C = +2.5 - 0.176 \times 5 = 1.62 \text{ V}$$

Since  $V_C > V_B$ , active-mode operation is verified.

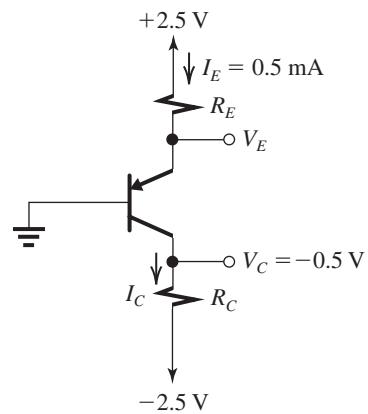**6.32**

From the figure we see that  $V_C = -0.5 \text{ V}$  is lower than the base voltage ( $V_B = 0 \text{ V}$ ); thus the transistor will be operating in the active mode.

$$I_C = \alpha I_E = \left( \frac{\beta}{\beta + 1} \right) I_E = \frac{100}{100 + 1} \times 0.5 = 0.495 \text{ mA}$$

$$R_C = \frac{V_C - (-2.5)}{I_C} = \frac{-0.5 + 2.5}{0.495} = 4.04 \text{ k}\Omega \simeq 4 \text{ k}\Omega$$

The transistor  $V_{EB}$  can be found from

$$V_{EB} = 0.64 + V_T \ln \left( \frac{0.5 \text{ mA}}{0.1 \text{ mA}} \right) = 0.68 \text{ V}$$

Thus,

$$V_E = +0.68 \text{ V}$$

and

$$R_E = \frac{2.5 - 0.68}{0.5} = 3.64 \text{ k}\Omega$$

The maximum allowable value for  $R_C$  while the transistor remains in the active mode corresponds to  $V_C = +0.4 \text{ V}$ . Thus,

$$R_{C\max} = \frac{0.4 - (-2.5)}{0.495} = 5.86 \text{ k}\Omega$$

**6.33** Refer to Fig. 6.15(a) with  $R_C = 5.1 \text{ k}\Omega$  and  $R_E = 6.8 \text{ k}\Omega$ . Assuming  $V_{BE} \simeq 0.7 \text{ V}$ , then  $V_E = -0.7 \text{ V}$ , and

$$I_E = \frac{-0.7 - (-15)}{6.8} = 2.1 \text{ mA}$$

$$I_C = \alpha I_E \simeq 2.1 \text{ mA}$$

$$V_C = 15 - 2.1 \times 5.1 \simeq 4.3 \text{ V}$$

**6.34** Refer to the circuit in Fig. P6.34. Since  $V_C = 0.5 \text{ V}$  is greater than  $V_B$ , the transistor will be operating in the active mode. The transistor  $V_{BE}$  can be found from

$$V_{BE} = 0.8 + 0.025 \ln \left( \frac{0.2 \text{ mA}}{1 \text{ mA}} \right) = 0.76 \text{ V}$$

Thus,

$$V_E = -0.76 \text{ V}$$

$$I_E = \frac{I_C}{\alpha} = I_C \left( \frac{\beta + 1}{\beta} \right) = 0.2 \times \frac{101}{100} = 0.202 \text{ mA}$$

The required value of  $R_E$  can be found from

$$R_E = \frac{V_E - (-1.5)}{I_E}$$

$$R_E = \frac{-0.76 + 1.5}{0.202} = 3.66 \text{ k}\Omega$$

To establish  $V_C = 0.5 \text{ V}$ , we select  $R_C$  according to

$$R_C = \frac{1.5 - 0.5}{0.2} = 5 \text{ k}\Omega$$

# Assignment Project Exam Help

# https://powcoder.com


# Add WeChat powcoder

**6.35**

(a)

$$\textcircled{4} \quad I_C = \alpha \times 0.26 = 0.98 \times 0.26 \\ = 0.255 \text{ mA}$$
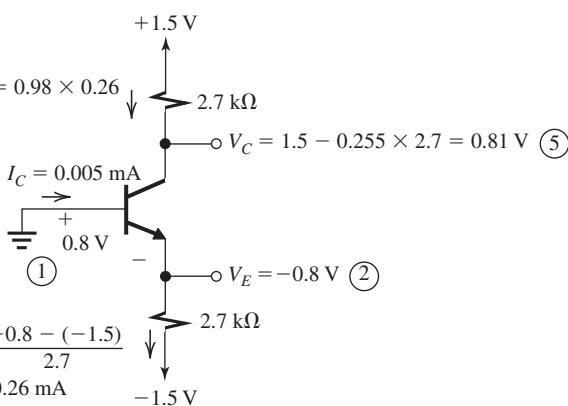
$$\textcircled{6} \quad I_B = I_E - I_C = 0.005 \text{ mA}$$



(b)

$$\textcircled{3} \quad I_E = \frac{1.5 - 0.8}{2} \\ = 0.35 \text{ mA}$$

$$\textcircled{6} \quad I_B = I_E - I_C \quad \textcircled{1} \quad 0.8 \text{ V} \\ = 0.007 \text{ mA}$$

$$\textcircled{4} \quad I_C = \frac{0.8}{10} = 0.08 \text{ mA} \quad \textcircled{2} \quad 0.81 \text{ V} \\ = 0.343 \text{ mA}$$

$$\textcircled{3} \quad I_E = \frac{3 - 1.8}{10} = 0.12 \text{ mA}$$

$$\textcircled{6} \quad I_B = I_C/50 = 2.4 \mu\text{A}$$

$$\textcircled{4} \quad I_C = \alpha \times 0.12 \\ = 0.98 \times 0.12 \\ = 0.118 \text{ mA}$$

(d)

$$\textcircled{4} \quad I_C = \alpha \times 0.15 = 0.147 \text{ mA}$$

$$\textcircled{6} \quad I_B = \frac{0.15}{50} = 3 \mu\text{A}$$

$$\textcircled{1} \quad I_B = 0.8 \text{ V}$$

$$\textcircled{3} \quad I_E = \frac{V_E}{4.7} \\ = \frac{0.7}{4.7} = 0.15 \text{ mA}$$

In all circuits shown in Fig. P6.35, we assume active-mode operation and verify that this is the case at the end of the solution. The solutions are

indicated on the corresponding circuit diagrams; the order of the steps is shown by the circled numbers.

# Assignment Project Exam Help


(c) <https://powcoder.com>

Add WeChat powcoder

**6.36**  $I_{CBO}$  approximately doubles for every  $10^{\circ}\text{C}$  rise in temperature. A change in temperature from  $25^{\circ}\text{C}$  to  $125^{\circ}\text{C}$ —that is, an increase of  $100^{\circ}\text{C}$ —results in 10 doublings or, equivalently, an increase by a factor of  $2^{10} = 1024$ . Thus  $I_{CBO}$  becomes

$$I_{CBO} = 10 \text{ nA} \times 1024 = 10.24 \mu\text{A}$$

**6.37**

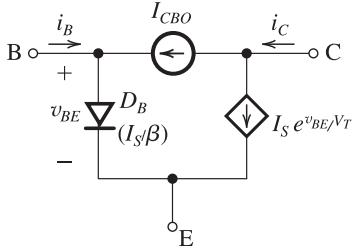

From the figure we can write

$$I_B = \left( \frac{I_S}{\beta} \right) e^{v_{BE}/V_T} - I_{CBO} \quad (1)$$

$$I_C = I_S e^{v_{BE}/V_T} + I_{CBO} \quad (2)$$

$$I_E = I_S \left( 1 + \frac{1}{\beta} \right) e^{v_{BE}/V_T} \quad (3)$$

When the base is left open circuited,  $i_B = 0$  and Eq. (1) yields

$$I_{CBO} = \left( \frac{I_S}{\beta} \right) e^{v_{BE}/V_T}$$

or equivalently,

$$I_S e^{v_{BE}/V_T} = \beta I_{CBO} \quad (4)$$

Substituting for  $I_S e^{v_{BE}/V_T}$  in Eqs. (2) and (3) gives

$$i_C = i_E = (\beta + 1) I_{CBO}$$

**6.38** Since the BJT is operating at a constant emitter current, its  $|V_{BE}|$  decreases by 2 mV for every  $^{\circ}\text{C}$  rise in temperature. Thus,

$$|V_{BE}| \text{ at } 0^{\circ}\text{C} = 0.7 + 0.002 \times 25 = 0.75 \text{ V}$$

$$|V_{BE}| \text{ at } 100^{\circ}\text{C} = 0.7 - 0.002 \times 75 = 0.55 \text{ V}$$

**6.39** (a) If the junction temperature rises to  $50^{\circ}\text{C}$ , which is an increase of  $30^{\circ}\text{C}$ , the EB voltage decreases to

$$v_{EB} = 692 - 2 \times 30 = 632 \text{ mV}$$

(b) First, we evaluate  $V_T$  at  $20^{\circ}\text{C}$  and at  $50^{\circ}\text{C}$ :

$$V_T = \frac{kT}{q}$$

where  $k = 8.62 \times 10^{-5} \text{ eV/K}$ .

Thus,

$$\text{At } 20^{\circ}\text{C}, T = 293 \text{ K and } V_T = 8.62 \times 10^{-5} \times 293 = 25.3 \text{ mV}$$

$$\text{At } 50^{\circ}\text{C}, T = 323 \text{ K and } V_T = 8.62 \times 10^{-5} \times 323 = 27.8 \text{ mV}$$

If the transistor is operated at  $v_{BE} = 700 \text{ mV}$ , then

(i) At  $20^{\circ}\text{C}$ ,  $i_E$  becomes

$$i_E = 0.5e^{(700-692)/25.3} = 0.69 \text{ mA}$$

(ii) At  $50^{\circ}\text{C}$ ,  $i_E$  becomes

$$i_E = 0.5e^{(700-632)/27.8} = 5.77 \text{ mA}$$

**6.40**  $v_{BE} = 0.7 \text{ V}$  at  $i_C = 10 \text{ mA}$

For  $v_{BE} = 0.5 \text{ V}$ ,

$$i_C = 10e^{(0.5-0.7)/0.025} = 3.35 \mu\text{A}$$

At a current  $I_C$  and a BE voltage  $V_{BE}$ , the slope of the  $i_C-v_{BE}$  curve is  $I_C/V_T$ . Thus

$$\text{Slope at } V_{BE} \text{ of } 700 \text{ mV} = \frac{0 \text{ mA}}{25 \text{ mV}} = 400 \text{ mA/V}$$

$$\text{Slope at } V_{BE} \text{ of } 500 \text{ mV} = \frac{3.35 \mu\text{A}}{25 \text{ mV}} = 0.134 \text{ mA/V}$$

$$\text{Ratio of slopes} = \frac{400}{0.134} \simeq 3000$$

**6.41** (Use Eq. (6.18))

$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

with  $I_S = 10^{-15} \text{ A}$  and  $V_A = 100 \text{ V}$ , to get

$$i_C = 10^{-15} e^{v_{BE}/0.025} \left( 1 + \frac{v_{CE}}{100} \right)$$


$v_{BE}$	0.65 V	0.70 V	0.72 V	0.73 V	0.74 V
$v_{CE}$ (V)	$i_C$ (mA)				
0	0.196	1.45	3.21	4.81	7.16
15	0.225	1.67	3.70	5.52	8.24

To find the intercept of the straight-line characteristics on the  $i_c$  axis, we substitute  $v_{CE} = 0$  and evaluate


$$i_C = 10^{-15} e^{v_{BE}/V_T} \text{ A}$$

for the given value of  $v_{BE}$ . The slope of each straight line is equal to this value divided by 100 V ( $V_A$ ). Thus we obtain

$v_{BE}$ (V)	0.65	0.70	0.72	0.73	0.74
Intercept (mA)	0.2	1.45	3.22	4.80	7.16
Slope (mA/V)	0.002	0.015	0.032	0.048	0.072

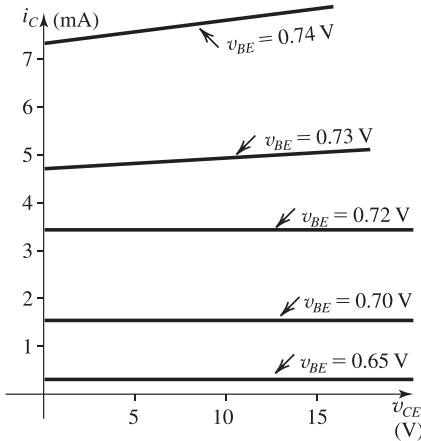

6.42

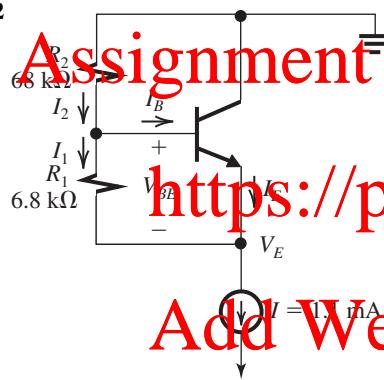

At  $25^\circ\text{C}$ , assume  $I_E = 1 \text{ mA}$ . Thus,

$$V_{BE} = 0.68 \text{ V}$$

$$I_1 = \frac{V_{BE}}{R_1} = \frac{0.68 \text{ V}}{6.8 \text{ k}\Omega} = 0.1 \text{ mA}$$

$$I_E = I - I_1 = 1.1 - 0.1 = 1 \text{ mA}$$

which is the value assumed.

$$I_2 = I_1 + I_B = I_1 + \frac{I_E}{\beta + 1}$$

$$= 0.1 + \frac{1}{101} = 0.11 \text{ mA}$$

Note that the currents in  $R_1$  and  $R_2$  differ only by the small base current, 0.01 mA. Had  $I_1$  and  $I_2$  been equal, then we would have had

$$I_1 R_1 = V_{BE}$$

$$I_2 R_2 \simeq I_1 R_2 = V_{BE} \frac{R_2}{R_1}$$

$$V_E = -(I_1 R_1 + I_2 R_2)$$

$$= -V_{BE} \left( 1 + \frac{R_2}{R_1} \right) \quad (1)$$

$$= -V_{BE} \left( 1 + \frac{6.8}{0.68} \right) = -11 \text{ V}$$

which gives this circuit the name “ $V_{BE}$  multiplier.” A more accurate value of  $V_E$  can be obtained by taking  $I_B$  into account:

$$\begin{aligned} V_E &= -(I_1 R_1 + I_2 R_2) \\ &= - \left( V_{BE} + \frac{R_2}{R_1} V_{BE} + I_B R_2 \right) \\ &= - \left( 1 + \frac{R_2}{R_1} \right) V_{BE} - I_B R_2 \\ &= -7.48 - 0.01 \times 68 = -8.16 \text{ V} \end{aligned} \quad (2)$$

As temperature increases, an approximate estimate for the temperature coefficient of  $V_E$  can be obtained by assuming that  $I_E$  remains constant and ignoring the temperature variation of  $\beta$ . Thus, we would be neglecting the temperature change of the  $(I_B R_2)$  terms in Eq. (2). From Eq. (2) we can obtain the temperature coefficient of  $V_E$  by utilizing the fact the  $V_{BE}$  changes by  $-2.2 \text{ mV}/^\circ\text{C}$ . Thus,

$$\begin{aligned} \text{Temperature coefficient of } V_E \\ &= - \left( 1 + \frac{R_2}{R_1} \right) \times -2.2 \\ &= -11 \times -2.2 = +24.2 \text{ mV}/^\circ\text{C} \end{aligned}$$

At  $75^\circ\text{C}$  which is a temperature increase of  $50^\circ\text{C}$ ,

$$V_E = -8.16 + 24.2 \times 50 = -6.95 \text{ V}$$

As a check on our assumption of constant  $I_E$ , let us find the value of  $I_E$  at  $75^\circ\text{C}$ :

$$\begin{aligned} I_E(75^\circ\text{C}) &= \frac{V_{BE}(75^\circ\text{C})}{R_1} \\ &= \frac{0.68 - 2.2 \times 10^{-3} \times 50}{6.8} \\ &= 0.084 \text{ mA} \end{aligned}$$

$$I_E(75^\circ\text{C}) = I - I_1(75^\circ\text{C})$$

$$= 1.1 - 0.084 = 1.016 \text{ mA}$$

which is reasonably close to the assumed value of 1 mA.

6.43  $r_o = 1/\text{slope}$

$$= 1/(0.8 \times 10^{-5})$$

$$= 125 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C}$$

$$125 \text{ k}\Omega = \frac{V_A}{1 \text{ mA}} \Rightarrow V_A = 125 \text{ V}$$

At  $I_C = 10 \text{ mA}$ ,

$$r_o = \frac{V_A}{I_C} = \frac{125 \text{ V}}{10 \text{ mA}} = 12.5 \text{ k}\Omega$$


$$6.44 \quad r_o = \frac{V_A}{I_C} = \frac{50 \text{ V}}{I_C}$$

Thus,

$$\text{At } I_C = 1 \text{ mA}, \quad r_o = \frac{50 \text{ V}}{1 \text{ mA}} = 50 \text{ k}\Omega$$

$$\text{At } I_C = 100 \mu\text{A}, \quad r_o = \frac{50 \text{ V}}{0.1 \text{ mA}} = 500 \text{ k}\Omega$$

6.45

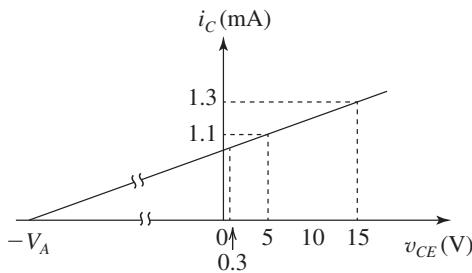

Slope of  $i_C-v_{CE}$  line corresponding to

$$v_{BE} = 710 \text{ mV is} \quad 6.47 \quad \beta = \frac{i_C}{i_B} = \frac{1 \text{ mA}}{0.1 \text{ mA}} = 100$$

$$\text{Slope} = \frac{1.3 - 1.1}{15 - 5} = \frac{0.2 \text{ mA}}{10 \text{ V}} = 0.02 \text{ mA/V}$$

Near saturation,  $V_{CE} = 0.3 \text{ V}$ , thus

$$i_C = 1.1 - 0.02 \times (5 - 0.3) = 1.006 \simeq 1 \text{ mA}$$

$$i_C \text{ will be } 1.2 \text{ mA at}$$

$$v_{CE} = 5 + \frac{1.2 - 1.1}{0.02} = 10 \text{ V}$$

The intercept of the  $i_C-v_{CE}$  straight line on the  $i_C$  axis will be at

$$i_C = 1.1 - 5 \times 0.02 = 1 \text{ mA}$$

Thus, the Early voltage is obtained as



$$\text{Slope} = \frac{i_C(\text{at } v_{CE} = 0)}{V_A}$$

$$\Rightarrow V_A = \frac{1}{0.02} = 50 \text{ V}$$

$$r_o = \frac{V_A}{I_C} = \frac{50 \text{ V}}{1 \text{ mA}} = 50 \text{ k}\Omega$$

which is the inverse of the slope of the  $i_C-v_{CE}$  line.

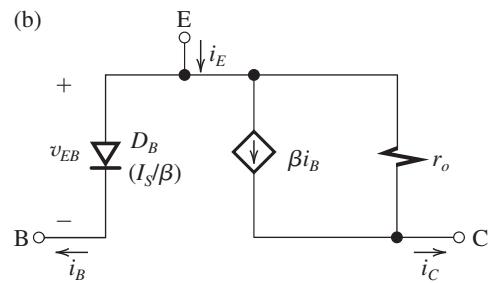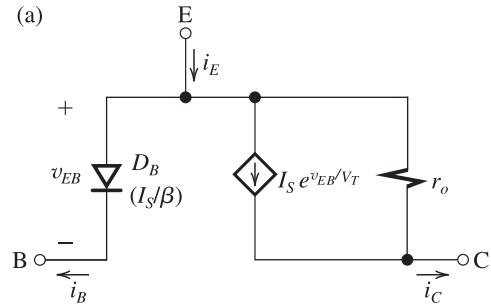6.46 The equivalent circuits shown in the figure correspond to the circuits in Fig. 6.19.



where

$$r_o = \frac{V_A}{I_C} = \frac{100}{1} = 100 \text{ k}\Omega$$

Thus,

$$\Delta i_C = 2 \times 80 + \frac{2}{100} \times 10^3 = 180 \mu\text{A}$$

$$= 0.18 \text{ mA}$$

6.48 Refer to the circuit in Fig. P6.48.

(a) For active-mode operation with  $V_C = 2 \text{ V}$ :

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{10 - 2}{1} = 8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{8}{50} = 0.16 \text{ mA}$$

$$V_{BB} = I_B R_B + V_{BE}$$

$$= 0.16 \times 10 + 0.7 = 2.3 \text{ V}$$

(b) For operation at the edge of saturation:

$$V_{CE} = 0.3 \text{ V}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 0.3}{1} = 9.7 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{9.7}{50} = 0.194 \text{ mA}$$

$$V_{BB} = I_B R_B + V_{BE}$$

$$= 0.194 \times 10 + 0.7 = 2.64 \text{ V}$$

(c) For operation deep in saturation with  $\beta_{\text{forced}} = 10$ :

$$V_{CE} = 0.2 \text{ V}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 0.2}{1} = 9.8 \text{ mA}$$

$$I_B = \frac{I_C}{\beta_{\text{forced}}} = \frac{9.8}{10} = 0.98 \text{ mA}$$

$$V_{BB} = I_B R_B + V_{BE}$$

$$= 0.98 \times 10 + 0.7 = 10.5 \text{ V}$$

**6.49** Refer to the circuit in Fig. P6.48 (with  $V_{BB} = V_{CC}$ ) and to the BJT equivalent circuit of Fig. 6.21.

$$I_C = \frac{V_{CC} - 0.2}{R_C}$$

$$I_B = \frac{V_{CC} - 0.7}{R_B}$$

$$\beta_{\text{forced}} \equiv \frac{I_C}{I_B}$$

Thus,

$$\beta_{\text{forced}} = \left( \frac{V_{CC} - 0.2}{V_{CC} - 0.7} \right) \left( \frac{R_B}{R_C} \right) \quad (1)$$

$$P_{\text{dissipated}} = V_{CC}(I_C + I_B)$$

$$= V_{CC}(\beta_{\text{forced}} I_B + I_B)$$

$$= (\beta_{\text{forced}} + 1)V_{CC}I_B \quad (2)$$

For  $V_{CC} = 5 \text{ V}$  and  $\beta_{\text{forced}} = 10$  and

$P_{\text{dissipated}} \leq 20 \text{ mW}$ , we can proceed as follows.

Using Eq. (1) we can determine  $(R_B/R_C)$ :

$$10 = \left( \frac{5 - 0.2}{5 - 0.7} \right) \left( \frac{R_B}{R_C} \right)$$

$$\Rightarrow \frac{R_B}{R_C} = 8.96 \quad (3)$$

Using Eq. (2), we can find  $I_B$ :

$$(10 + 1) \times 5 \times I_B \leq 20 \text{ mW}$$

$$\Rightarrow I_B \leq 0.36 \text{ mA}$$

Thus,

$$\frac{V_{CC} - 0.7}{R_B} \leq 0.36 \text{ mA}$$

$$\Rightarrow R_B \geq 11.9 \text{ k}\Omega$$

From the table of 1% resistors in Appendix J we select

$$R_B = 12.1 \text{ k}\Omega$$

Substituting in Eq. (3), we have

$$R_C = 1.35 \text{ k}\Omega$$

From the table of 1% resistors in Appendix J we select

$$R_C = 1.37 \text{ k}\Omega$$

For these values:

$$I_C = \frac{5 - 0.2}{1.37} = 3.5 \text{ mA}$$

$$I_B = \frac{5 - 0.7}{12.1} = 0.36 \text{ mA}$$

Thus,

$$\beta_{\text{forced}} = \frac{3.5}{0.36} = 9.7$$


$$P_{\text{dissipated}} = V_{CC}(I_C + I_B)$$

$$= 5 \times 3.86 = 19.2 \text{ mW}$$

## Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

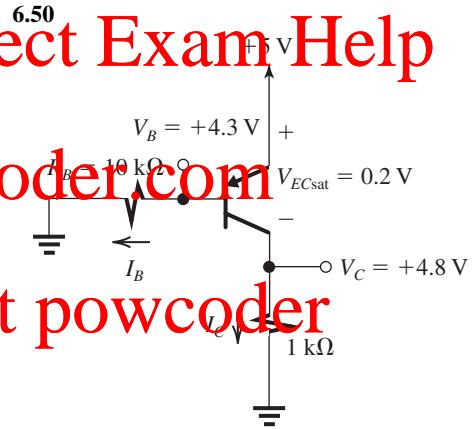

Assume saturation-mode operation. From the figure we see that

$$I_C = \frac{V_C}{1 \text{ k}\Omega} = \frac{4.8}{1} = 4.8 \text{ mA}$$

$$I_B = \frac{V_B}{R_B} = \frac{4.3}{10} = 0.43 \text{ mA}$$

Thus,

$$\beta_{\text{forced}} \equiv \frac{I_C}{I_B} = \frac{4.8}{0.43} = 11.2$$

Since 11.2 is lower than the transistor  $\beta$  of 50, we have verified that the transistor is operating in saturation, as assumed.

$$V_C = V_{CC} - V_{ECsat} = 5 - 0.2 = 4.8 \text{ V}$$

To operate at the edge of saturation,

$$V_{EC} = 0.3 \text{ V} \quad \text{and} \quad I_C/I_B = \beta = 50$$


Thus,

$$I_C = \frac{5 - 0.3}{1} = 4.7 \text{ mA}$$



$$I_B = \frac{I_C}{\beta} = \frac{4.7}{50} = 0.094 \text{ mA}$$

$$R_B = \frac{4.3}{I_B} = \frac{4.3}{0.094} = 45.7 \text{ k}\Omega$$

**6.51**

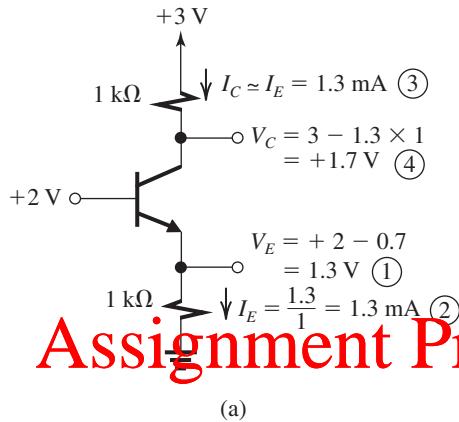

## Assignment Project Exam Help

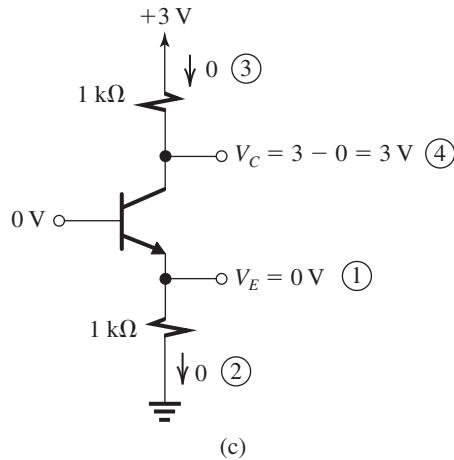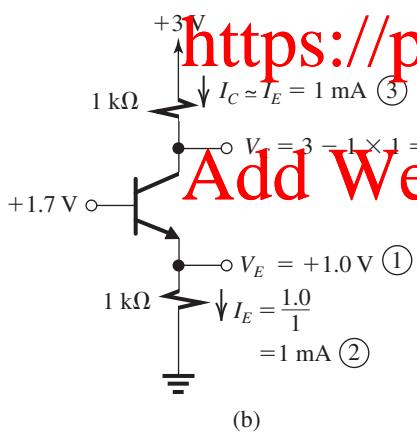

The analysis and the results are given on the circuit diagrams of Figs. 1 through 3. The circled numbers indicate the order of the analysis steps.

**6.52**

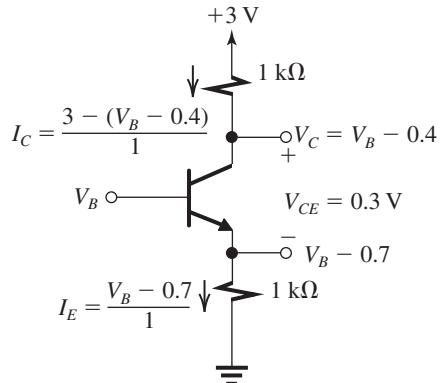


Figure 1

Figure 1 shows the circuit with the value of  $V_B$  that results in operation at the edge of saturation. Since  $\beta$  is very high,

$$\begin{aligned} I_C &\simeq I_E \\ \frac{3 - (V_B - 0.4)}{1} &= V_B - 0.7 \\ \Rightarrow V_B &= 2.05 \text{ V} \end{aligned}$$

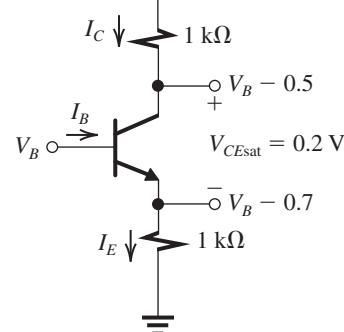


Figure 2

Figure 2 shows the circuit with the value of  $V_B$  that results in the transistor operating in saturation, with

$$I_E = \frac{V_B - 0.7}{1} = V_B - 0.7$$

$$I_C = \frac{3 - (V_B - 0.5)}{1} = 3.5 - V_B$$

$$I_B = I_E - I_C = 2V_B - 4.2$$

For  $\beta_{\text{forced}} = 2$ ,

$$\frac{I_C}{I_B} = 2$$

$$\frac{3.5 - V_B}{2V_B - 4.2} = 2$$

$$\Rightarrow V_B = 2.38 \text{ V}$$

**6.53** Refer to the circuit in Fig. P6.53.

(a) For  $V_B = -1 \text{ V}$ ,

$$V_E = V_B - V_{BE} = -1 - 0.7 = -1.7 \text{ V}$$

$$I_E = \frac{V_E - (-3)}{1} = \frac{-1.7 + 3}{1} = 1.3 \text{ mA}$$

Assuming active-mode operation, we have

$$I_C = \alpha I_E \approx I_E = 1.3 \text{ mA}$$

$$V_C = +3 - I_C \times 1 = 3 - 1.3 = +1.7 \text{ V}$$

Since  $V_C > V_B - 0.4$ , the transistor is operating in the active mode, as assumed.

(b) For  $V_B = 0 \text{ V}$ ,

$$V_E = 0 - V_{BE} = -0.7 \text{ V}$$

$$I_E = \frac{-0.7 - (-3)}{1} = 2.3 \text{ mA}$$

Assuming operation in the active mode, we have

$$I_C = \alpha I_E \approx I_E = 2.3 \text{ mA}$$

$$V_C = +3 - I_C \times 1 = 3 - 2.3 = +0.7 \text{ V}$$

Since  $V_C > V_B - 0.4$ , the BJT is operating in the active mode, as assumed.

(c) For  $V_B = +1 \text{ V}$ ,

$$V_E = 1 - 0.7 = +0.3 \text{ V}$$

$$I_E = \frac{0.3 - (-3)}{1} = 3.3 \text{ mA}$$

Assuming operation in the active mode, we have

$$I_C = \alpha I_E \approx I_E = 3.3 \text{ mA}$$

$$V_C = 3 - 3.3 \times 1 = -0.3 \text{ V}$$

Now  $V_C < V_B - 0.4$ , indicating that the transistor is operating in saturation, and our original assumption is incorrect. It follows that

$$V_C = V_E + V_{CE\text{sat}}$$

$$= 0.3 + 0.2 = 0.5 \text{ V}$$

$$I_C = \frac{3 - V_C}{1} = \frac{3 - 0.5}{1} = 2.5 \text{ mA}$$

$$I_B = I_E - I_C = 3.3 - 2.5 = 0.8 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = \frac{2.5}{0.8} = 3.1$$

(d) When  $V_B = 0 \text{ V}$ ,  $I_E = 2.3 \text{ mA}$ . The emitter current becomes 0.23 mA at

$$V_B = -3 + 0.23 \times 1 + 0.7 = -2.07 \text{ V}$$

(e) The transistor will be at the edge of conduction when  $I_E \approx 0$  and  $V_{BE} = 0.5 \text{ V}$ , that is,

$$V_B = -3 + 0.5 = -2.5 \text{ V}$$

In this case,

$$V_E = -3 \text{ V}$$

$$V_C = +3 \text{ V}$$

(f) The transistor reaches the edge of saturation when  $V_{CE} = 0.3 \text{ V}$  but  $I_C = \alpha I_E \approx I_E$ :

$$V_E = V_B - 0.7$$

$$V_C = V_E + 0.3 = V_B - 0.4$$

$$I_C = \frac{3 - V_C}{1} = \frac{3 - V_B + 0.4}{1} = 3.4 - V_B$$

Since

$$\frac{I_C \approx I_E}{3.4 - V_B = V_B + 0.4}$$

$$V_B = 0.55 \text{ V}$$

For this value,

$$V_E = 0.55 - 0.7 = -0.15 \text{ V}$$

$$V_C = -0.15 + 0.3 = +0.15 \text{ V}$$

(g) For the transistor to operate in saturation with  $\beta_{\text{forced}} = 2$ ,

$$V_E = V_B - 0.7$$

$$I_E = \frac{V_B - 0.7 - (-3)}{1} = V_B + 2.3$$

$$V_C = V_E + V_{CE\text{sat}} = V_B - 0.7 + 0.2 = V_B - 0.5$$

$$I_C = \frac{3 - (V_B - 0.5)}{1} = 3.5 - V_B$$

$$I_B = I_E - I_C = 2 V_B - 1.2$$

$$\frac{I_C}{I_B} = \frac{3.5 - V_B}{2 V_B - 1.2} = 2$$

$$\Rightarrow V_B = +1.18 \text{ V}$$

**6.54 (a)  $V_B = 0 \text{ V}$**

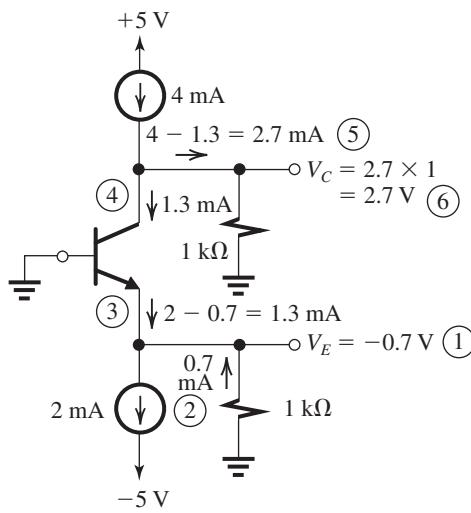


Figure 1

**(c)**

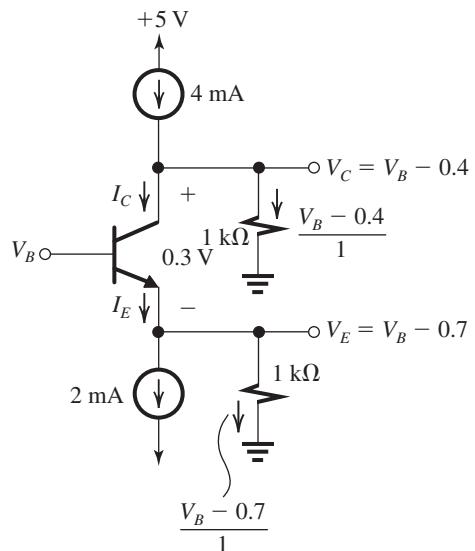


Figure 3

The analysis is shown on the circuit diagram in Fig. 1. The circled numbers indicate the order of the analysis steps.

**(b)** The transistor cuts off at the value of  $V_B$  that causes the 2-mA current of the current source feeding the emitter to flow through the 1 kΩ resistor connected between the emitter and ground. The circuit under these conditions is shown in Fig. 2.

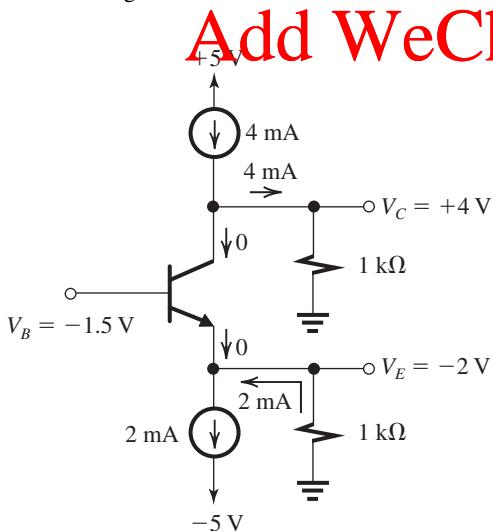


Figure 2

Observe that  $V_E = -2 \text{ mA} \times 1 \text{ k}\Omega = -2 \text{ V}$ ,  $I_E = 0$ , and  $V_B = V_E + 0.5 = -1.5 \text{ V}$ . Since  $I_C = 0$ , all the 4 mA supplied by the current source feeding the collector flows through the collector 1-kΩ resistor, resulting in  $V_C = +4 \text{ V}$ .

Figure 3 shows the transistor at the edge of saturation. Here  $V_B = 0.3 \text{ V}$  and  $I_C = \alpha I_E \simeq I_E$ . A node equation at the emitter gives

$$I_E = 2 + V_B - 0.7 = V_B + 1.3 \text{ mA}$$

A node equation at the collector gives

$$I_C = 4 - (V_B - 0.4) = 4.4 - V_B \text{ mA}$$

Imposing the condition  $I_C \simeq I_E$  gives

$$4.4 - V_B = V_B + 1.3$$

$$\Rightarrow V_B = +1.55 \text{ V}$$

Correspondingly,

$$V_E = +0.85 \text{ V}$$

$$V_C = +1.15 \text{ V}$$

**6.55**

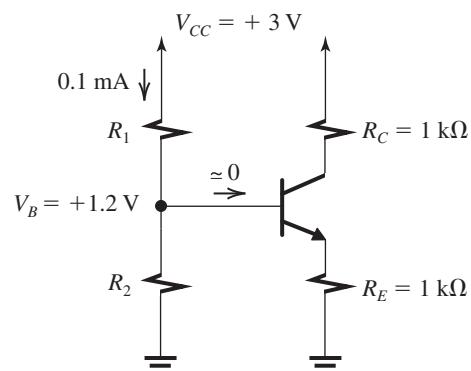


Figure 1

From Fig. 1 we see that

$$R_1 + R_2 = \frac{V_{CC}}{0.1 \text{ mA}} = \frac{3}{0.1} = 30 \text{ k}\Omega$$

$$V_{CC} \frac{R_2}{R_1 + R_2} = 1.2$$

$$3 \times \frac{R_2}{30} = 1.2$$

$$\Rightarrow R_2 = 12 \text{ k}\Omega$$

$$R_1 = 30 - 12 = 18 \text{ k}\Omega$$

For  $\beta = 100$ , to obtain the collector current, we replace the voltage divider with its Thévenin equivalent, consisting of

$$V_{BB} = 3 \times \frac{R_2}{R_1 + R_2} = 3 \times \frac{12}{18 + 12} = 1.2 \text{ V}$$

$$R_B = R_1 \parallel R_2 = 12 \parallel 18 = 7.2 \text{ k}\Omega$$

**6.56** Refer to the circuit in Fig. P6.56.

$$V_E = 1 \text{ V}$$

$$I_E = \frac{3 - 1}{5} = 0.4 \text{ mA}$$

$$V_B = V_E - 0.7 = 0.3 \text{ V}$$

$$I_B = \frac{V_B}{50 \text{ k}\Omega} = \frac{0.3}{50} = 0.006 \text{ mA}$$

$$I_C = I_E - I_B = 0.4 - 0.006 = 0.394 \text{ mA}$$

$$V_C = -3 + 5 \times 0.394 = -1.03 \text{ V}$$

Observe that  $V_C < V_B$ , confirming our implicit assumption that the transistor is operating in the active region.

$$\beta = \frac{I_C}{I_B} = \frac{0.394}{0.006} = 66$$

$$\alpha = \frac{I_C}{I_E} = \frac{0.394}{0.4} = 0.985$$

**6.57**

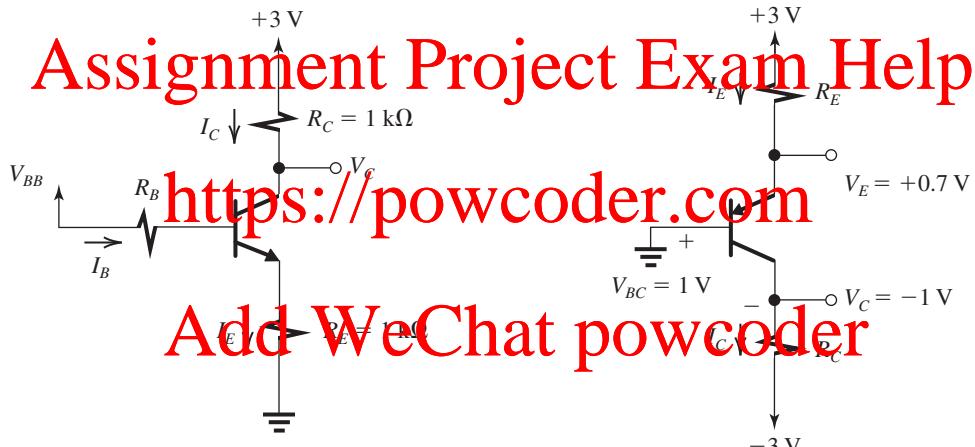


Figure 2

Refer to Fig. 2. Assuming active-mode operation, we can write a loop equation for the base-emitter loop:

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

$$1.2 = \frac{I_E}{\beta + 1} \times 7.2 + 0.7 + I_E \times 1$$

$$\Rightarrow I_E = \frac{1.2 - 0.7}{1 + \frac{7.2}{101}} = 0.47 \text{ mA}$$

$$I_C = \alpha I_E = 0.99 \times 0.47 = 0.46 \text{ mA}$$

$$V_C = +3 - 0.46 \times 1 = +2.54 \text{ V}$$

Since  $V_B = I_E R_E + V_{BE} = 0.47 + 0.7 = 1.17 \text{ V}$ , we see that  $V_C > V_B - 0.4$ , and thus the transistor is operating in the active region, as assumed.

Refer to the figure. To obtain  $I_E = 0.5 \text{ mA}$  we select  $R_E$  according to

$$R_E = \frac{3 - 0.7}{0.5} = 4.6 \text{ k}\Omega$$

To obtain  $V_C = -1 \text{ V}$ , we select  $R_C$  according to

$$R_C = \frac{-1 - (-3)}{0.5} = 4 \text{ k}\Omega$$

where we have utilized the fact that  $\alpha \simeq 1$  and thus  $I_C \simeq I_E = 0.5 \text{ mA}$ . From the table of 5% resistors in Appendix J we select


$$R_E = 4.7 \text{ k}\Omega \quad \text{and} \quad R_C = 3.9 \text{ k}\Omega$$

For these values,

$$I_E = \frac{3 - 0.7}{4.7} = 0.49 \text{ mA}$$

$$I_C \simeq I_E = 0.49 \text{ mA}$$

$$V_{BC} = 0 - V_C = -(-3 + 0.49 \times 3.9) = -1.1 \text{ V}$$

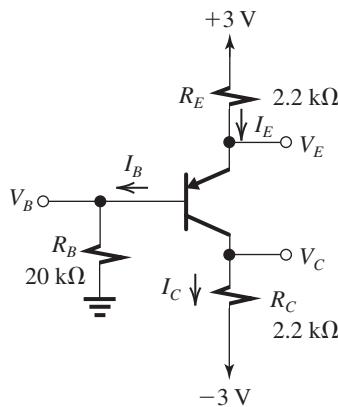
**6.58**

$$\frac{3 - 0.7}{2.2 + \frac{20}{41}} = \frac{3 - 0.7}{2.2 + \frac{100}{\beta + 1}}$$

$$\Rightarrow \frac{20}{41} = \frac{100}{\beta + 1}$$

$$\beta + 1 = \frac{410}{2} = 205$$

$$\beta = 204$$

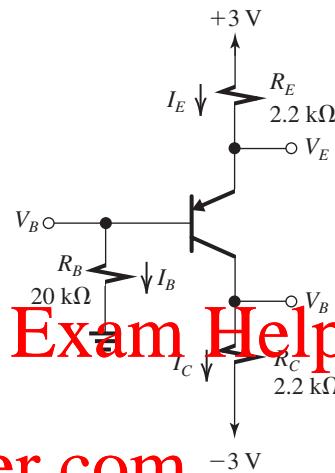**6.59**

Writing a loop equation for the EBJ loop, we have

$$3 = I_E R_E + V_{EB} + I_B R_B \quad (1)$$

$$= I_E \times 2.2 + 0.7 + \frac{I_E}{\beta + 1} \times 20$$

$$\Rightarrow I_E = \frac{3 - 0.7}{2.2 + \frac{20}{41}} = 0.86 \text{ mA}$$

$$V_E = 3 - 0.86 \times 2.2 = +1.11 \text{ V}$$

$$V_B = V_E - 0.7 = +0.41 \text{ V}$$

Assuming active-mode operation, we obtain

$$I_C = \alpha I_E = \frac{40}{41} \times 0.86 = 0.84 \text{ mA}$$

$$V_C = -3 + 0.84 \times 2.2 = -1.5 \text{ V}$$

Since  $V_C < V_B + 0.4$ , the transistor is operating in the active mode, as assumed. Now, if  $R_B$  is increased to 100 kΩ, the loop equation [Eq. (1)] yields

$$I_E = \frac{3 - 0.7}{2.2 + \frac{100}{41}} = 0.5 \text{ mA}$$

$$V_E = 3 - 0.5 \times 2.2 = +1.9 \text{ V}$$

$$V_B = V_E - V_{EB} = 1.9 - 0.7 = +1.2 \text{ V}$$


Assuming active-mode operation, we obtain

$$I_C = \alpha I_E = \frac{40}{41} \times 0.5 = 0.48 \text{ mA}$$

$$V_C = -3 + 0.48 \times 2.2 = -1.9 \text{ V}$$

Since  $V_C < V_B + 0.4$ , the transistor is operating in the active mode, as assumed.

If with  $R_B = 100 \text{ k}\Omega$ , we need the voltages to remain at the values obtained with  $R_B = 20 \text{ k}\Omega$ , the transistor must have a  $\beta$  value determined as follows. For  $I_E$  to remain unchanged,

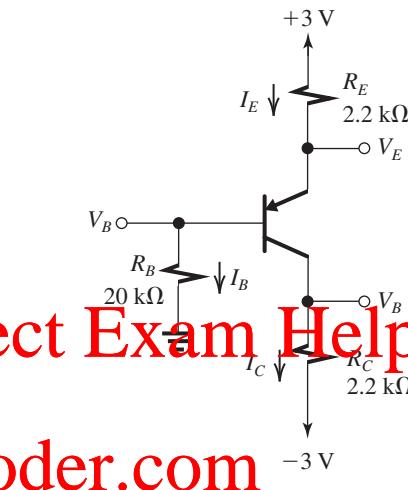**6.59**

Assume active-mode operation:

$$I_E = \frac{3 - V_{EB}}{R_B}$$

$$I_E = \frac{3 - 0.7}{2.2 + \frac{20}{51}} = 0.887 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{0.887}{51} = 0.017 \text{ mA}$$

$$I_C = I_E - I_B = 0.887 - 0.017 = 0.870 \text{ mA}$$

$$V_B = I_B R_B = 0.017 \times 20 = 0.34 \text{ V}$$


$$V_E = V_B + V_{EB} = 0.34 + 0.7 = 1.04 \text{ V}$$

$$V_C = -3 + I_C R_C = -3 + 0.87 \times 2.2 = -1.09 \text{ V}$$

Thus,  $V_C < V_B + 0.4$ , which means active-mode operation, as assumed. The maximum value of  $R_C$  that still guarantees active-mode operation is that which causes  $V_C$  to be 0.4 V above  $V_B$ : that is,  $V_C = 0.34 + 0.4 = 0.74 \text{ V}$ .

Correspondingly,

$$R_{C\max} = \frac{0.74 - (-3)}{0.87} = 4.3 \text{ k}\Omega$$

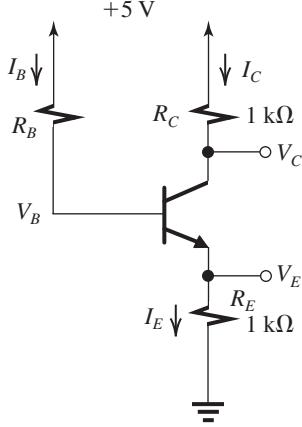**6.60**

A loop equation for the EB loop yields

$$5 = I_B R_B + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{5 - 0.7}{R_E + \frac{R_B}{\beta + 1}}$$

$$I_E = \frac{4.3}{1 + \frac{R_B}{101}}$$

(a) For  $R_B = 100 \text{ k}\Omega$ ,

$$I_E = \frac{4.3}{1 + \frac{100}{101}} = 2.16 \text{ mA}$$

$$V_E = I_E R_E = 2.16 \times 1 = 2.16 \text{ V}$$

$$V_B = V_E + 0.7 = 2.86 \text{ V}$$

Assuming active-mode operation, we obtain

$$I_C = \alpha I_E = 0.99 \times 2.16 = 2.14 \text{ mA}$$

$$V_C = 5 - 2.14 \times 1 = +2.86 \text{ V}$$

Since  $V_C > V_B - 0.4$ , the transistor is operating in the active region, as assumed.

(b) For  $R_B = 10 \text{ k}\Omega$ ,

$$I_E = \frac{4.3}{1 + \frac{10}{101}} = 3.91 \text{ mA}$$

$$V_E = 3.91 \times 1 = 3.91 \text{ V}$$

$$V_B = 3.91 + 0.7 = 4.61 \text{ V}$$

Assuming active-mode operation, we obtain

$$I_C = \alpha I_E = 0.99 \times 3.91 = 3.87 \text{ mA}$$

$$V_C = 5 - 3.87 = +1.13 \text{ V}$$

Since  $V_C < V_B - 0.4$ , the transistor is operating in saturation, contrary to our original assumption.

Therefore, we need to redo the analysis assuming saturation-mode operation, as follows:

$$V_B = V_E + 0.7$$

$$V_C = V_E + V_{CE\text{sat}} = V_E + 0.2$$

$$I_B = \frac{5 - V_B}{R_B} = \frac{5 - V_E - 0.7}{10} = \frac{4.3 - V_E}{10} \quad (1)$$

$$I_C = \frac{5 - V_C}{R_C} = \frac{5 - V_E - 0.2}{1} = 4.8 - V_E \quad (2)$$

$$I_E = \frac{V_E}{R_E} = \frac{V_E}{1} = V_E \quad (3)$$

Substituting from Eqs. (1), (2), and (3) into

$$I_E = I_B + I_C$$

gives

$$V_E = 0.43 - 0.1 V_E + 4.8 - V_E$$

$$\Rightarrow V_E = 2.5 \text{ V}$$

$$V_C = 2.7 \text{ V}$$

$$V_B = 3.2 \text{ V}$$

$$I_B = \frac{5 - 3.2}{10} = 0.18 \text{ mA}$$

$$I_C = \frac{5 - 2.7}{1} = 2.3 \text{ mA}$$

Thus,

$$\frac{I_C}{I_B} = \frac{2.3}{0.18} = 12.8$$

which is lower than the value of  $\beta$ , verifying saturation-mode operation.

(c) For  $R_B = 1 \text{ k}\Omega$ , we assume saturation-mode operation:

$$V_B = V_E + 0.7$$

$$V_C = V_E + 0.2$$

$$I_B = \frac{5 - (V_E + 0.7)}{1} = 4.3 - V_E$$

$$I_C = \frac{5 - (V_E + 0.2)}{1} = 4.8 - V_E$$

$$I_E = \frac{V_E}{1} = V_E$$

These values can be substituted into

$$I_E = I_B + I_C$$

to obtain

$$V_E = 4.3 - V_E + 4.8 - V_E$$

$$\Rightarrow V_E = 3 \text{ V}$$

$$V_B = 3.7 \text{ V}$$

$$V_C = 3.2 \text{ V}$$

Now checking the currents,

$$I_B = \frac{5 - 3.7}{1} = 1.3 \text{ mA}$$

$$I_C = \frac{5 - 3.2}{1} = 1.8 \text{ mA}$$

Thus, the transistor is operating at a forced  $\beta$  of

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = \frac{1.8}{1.3} = 1.4$$




which is much lower than the value of  $\beta$ , confirming operation in saturation.

# Assignment Project Exam Help


<https://powcoder.com>

# Add WeChat powcoder

## 6.61

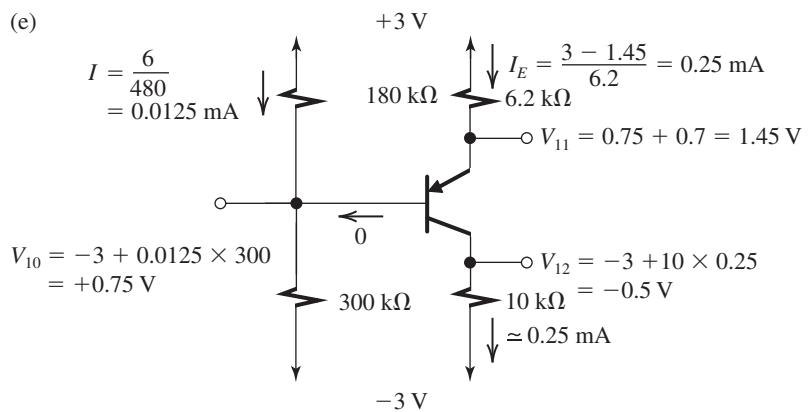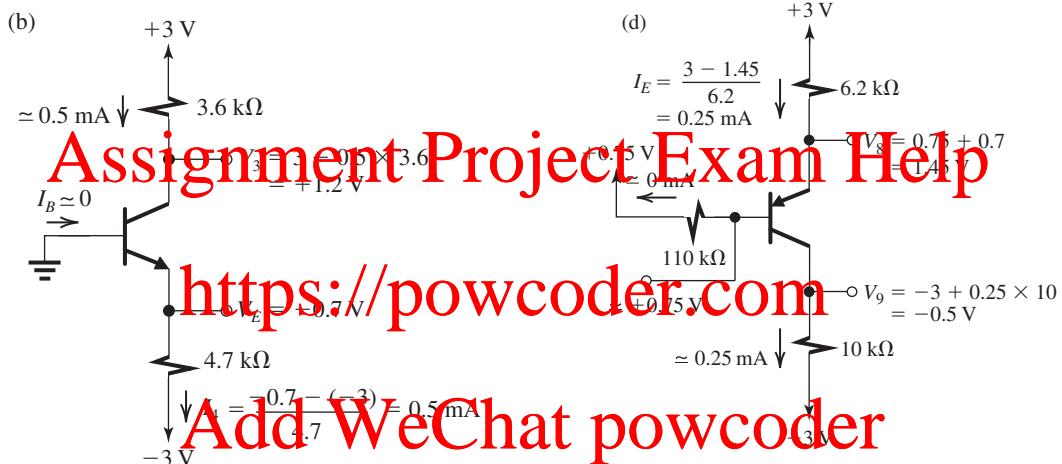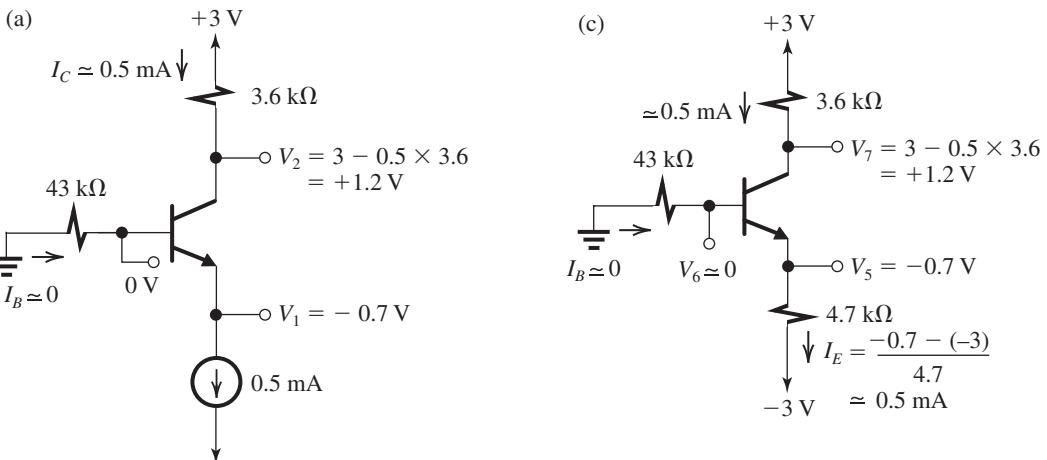

For the solutions and answers to parts (a) through (e), see the corresponding circuit diagrams.

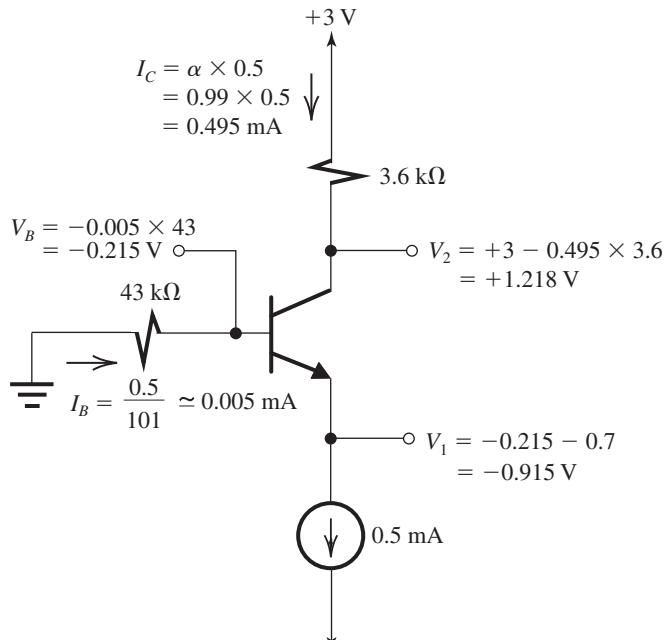**6.62 (a)**


## Assignment Project Exam Help

See solution and answer on the figure, which corresponds to Fig. P6.61(a).


<https://powcoder.com>

**(b)**

## Add WeChat powcoder

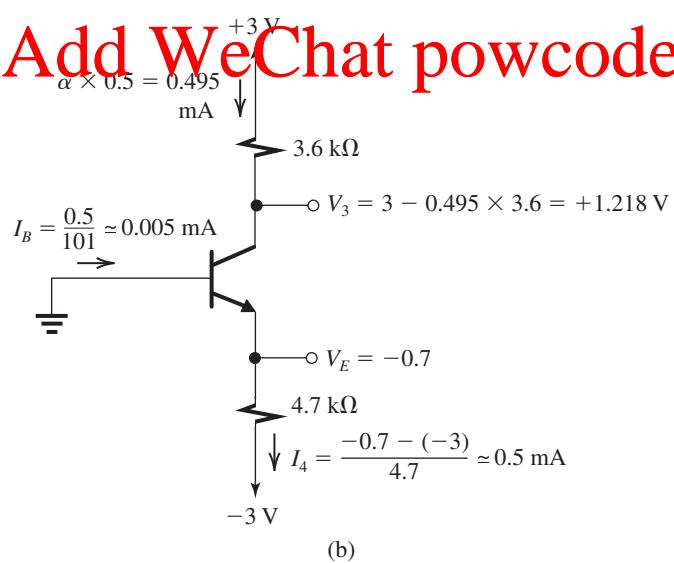

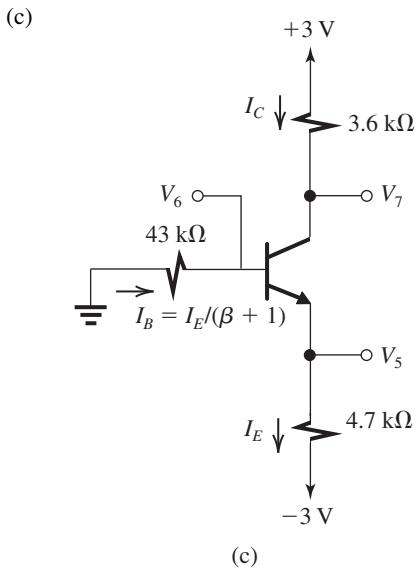See solution and answer on the figure, which corresponds to Fig. P6.61(b).



Writing an equation for the loop containing the EBJ of the transistor leads to

$$I_E = \frac{3 - 0.7}{43} = 0.449 \text{ mA}$$


$$V_5 = -3 + 0.449 \times 4.7 = -0.9 \text{ V}$$

$$V_6 = -0.9 + 0.7 = -0.2 \text{ V}$$

$$I_C = \alpha I_E = 0.99 \times 0.449 = 0.444 \text{ mA}$$

$$V_7 = 3 - 0.444 \times 3.6 = +1.4 \text{ V}$$

(d)

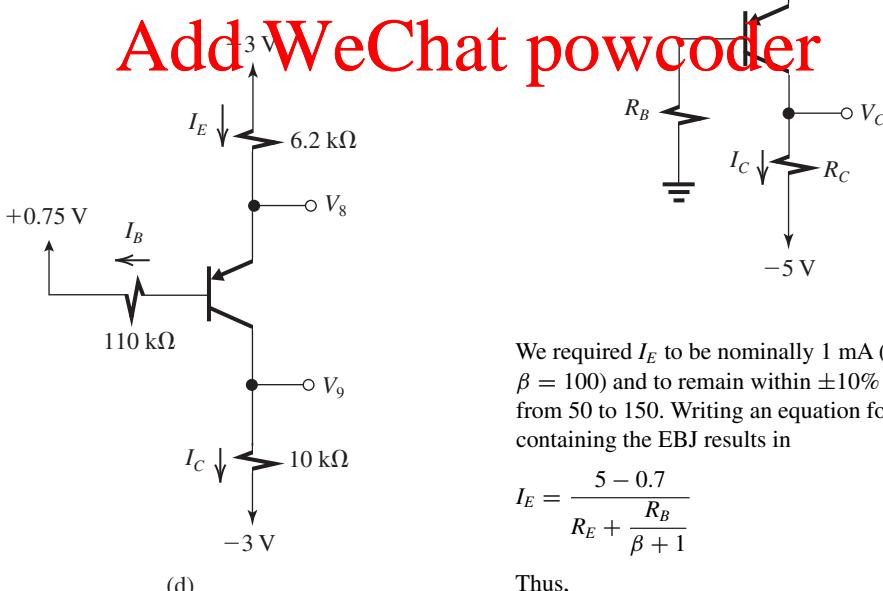

An equation for the loop containing the EBJ of the transistor yields

$$I_E = \frac{3 - 0.75 - 0.7}{6.2 + \frac{110}{101}} = 0.213 \text{ mA}$$

$$V_8 = +3 - 0.213 \times 6.2 = +1.7 \text{ V}$$

$$I_C = \alpha I_E = 0.99 \times 0.213 = 0.21 \text{ mA}$$

$$V_9 = -3 + 0.21 \times 10 = -0.9 \text{ V}$$

(e) See figure on next page.

First, we use Thévenin's theorem to replace the voltage divider feeding the base with  $V_{BB}$  and  $R_B$ :

$$V_{BB} = -3 + \frac{6}{480} \times 300 = +0.75 \text{ V}$$

$$R_B = 180 \parallel 300 = 112.5 \text{ k}\Omega$$

Next we write an equation for the loop containing the EBJ to obtain

$$I_E = \frac{3 - 0.75 - 0.7}{6.2 + \frac{112.5}{101}} = 0.212 \text{ mA}$$


$$V_{11} = +3 - 0.212 \times 6.2 = +1.7 \text{ V}$$

$$V_{10} = 1.7 - 0.7 = +1 \text{ V}$$

$$I_C = \alpha I_E = 0.99 \times 0.212 = 0.21 \text{ mA}$$

$$V_{12} = -3 + 0.21 \times 10 = -0.9 \text{ V}$$

### 6.63

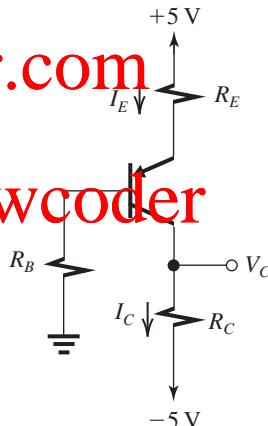

We required  $I_E$  to be nominally 1 mA (i.e., at  $\beta = 100$ ) and to remain within  $\pm 10\%$  as  $\beta$  varies from 50 to 150. Writing an equation for the loop containing the EBJ results in


$$I_E = \frac{5 - 0.7}{R_E + \frac{R_B}{\beta + 1}}$$

Thus,

$$\frac{4.3}{R_E + \frac{R_B}{101}} = 1 \quad (1)$$

$$\frac{4.3}{R_E + \frac{R_B}{51}} = I_{E\min} \quad (2)$$

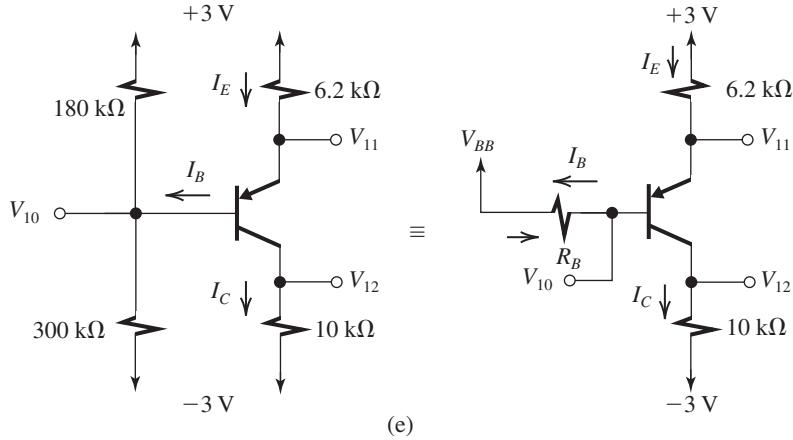This figure belongs to Problem 6.62, part (e).



$$\frac{4.3}{R_E + \frac{R_B}{151}} = I_{E\max} \quad (3)$$

If we set  $I_{E\min} = 0.9$  mA and solve Eqs. (1) and (2) simultaneously, we obtain

$$R_E = 3.1 \text{ k}\Omega$$

$$R_B = 49.2 \text{ k}\Omega$$

Substituting these values in Eqs. (2) and (3) gives

$$I_{E\min} = 0.9 \text{ mA}$$

$$I_{E\max} = 1.04 \text{ mA}$$

Obviously, this is an acceptable design.

Alternatively, if we set  $I_{E\max}$  in Eq. (3) to 1.1 mA and solve Eqs. (1) and (3) simultaneously, we obtain

$$R_E = 3.1 \text{ k}\Omega$$

$$R_B = 119.2 \text{ k}\Omega$$

Substituting these values in Eqs. (2) and (3) gives

$$I_{E\min} = 0.8 \text{ mA}$$

$$I_{E\max} = 1.1 \text{ mA}$$

Obviously this is not an acceptable design ( $I_{E\min}$  is 20% lower than nominal).

Therefore, we shall use the first design.

Specifying the resistor values to the nearest kilohm results in

$$R_E = 4 \text{ k}\Omega$$

$$R_B = 50 \text{ k}\Omega$$

To obtain the value of  $R_C$ , we note that at the nominal emitter current value of 1 mA,

$$V_C = -1 \text{ V},$$

$$I_C = \alpha I_E = 0.99 \text{ mA}$$

$$R_C = \frac{-1 - (-5)}{0.99} = 4.04 \text{ k}\Omega$$

Specified to the nearest kilohm,

$$R_C = 4 \text{ k}\Omega$$

Finally, for our design we need to determine the range obtained for collector current and collector voltage for  $\beta$  ranging from 50 to 150 with a nominal value of 100. We compute the nominal value of  $I_E$  from

$$I_{E\text{nominal}} = \frac{4.3}{4 + \frac{50}{101}} = 0.96 \text{ mA}$$

We utilize Eqs. (2) and (3) to compute  $I_{E\min}$  and  $I_{E\max}$ ,

$$I_{E\min} = \frac{4.3}{4 + \frac{50}{51}} = 0.86 \text{ mA}$$

$$I_{E\max} = \frac{4.3}{4 + \frac{50}{151}} = 0.99 \text{ mA}$$

Thus,

$$\frac{I_{E\max}}{I_{E\text{nominal}}} = \frac{0.99}{0.96} = 1.03$$

$$\frac{I_{E\min}}{I_{E\text{nominal}}} = \frac{0.86}{0.96} = 0.9$$

which meet our specifications. The collector currents are

$$I_{C\text{nominal}} = 0.99 \times 0.96 = 0.95 \text{ mA}$$

$$I_{C\min} = 0.99 \times 0.86 = 0.85 \text{ mA}$$


$$I_{C\max} = 0.99 \times 0.99 = 0.98 \text{ mA}$$

and the collector voltages are

$$V_{C\text{nominal}} = -5 + 0.95 \times 4 = -1.2 \text{ V}$$

$$V_{C\min} = -5 + 0.85 \times 4 = -1.6 \text{ V}$$

$$V_{C\max} = -5 + 0.98 \times 4 = -1.1 \text{ V}$$

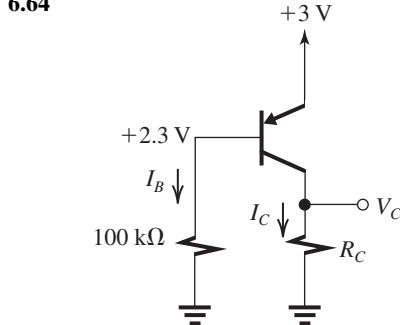**6.64**

$$I_B = \frac{2.3 \text{ V}}{100 \text{ k}\Omega} = 0.023 \text{ mA}$$

Since  $V_C = 2 \text{ V}$  is lower than  $V_B$ , which is  $+2.3 \text{ V}$ , the transistor will be operating in the active mode. Thus,

$$I_C = \beta I_B = 50 \times 0.023 = 1.15 \text{ mA}$$

To obtain  $V_C = 2 \text{ V}$ , we select  $R_C$  according to

$$R_C = \frac{V_C}{I_C} = \frac{2 \text{ V}}{1.15 \text{ mA}} = 1.74 \text{ k}\Omega$$

Now, if the transistor is replaced with another having  $\beta = 100$ , then

$$I_C = 100 \times 0.023 = 2.3 \text{ mA}$$

which would imply

$$V_C = 2.3 \times 1.74 = 4 \text{ V}$$

which is impossible because the base is at  $2.3 \text{ V}$ .

Thus the transistor must be in the saturation mode and

$$V_C = V_E - V_{ECsat}$$

$$= 3 - 0.2 = 2.8 \text{ V}$$

open circuited. The circuit is shown in Fig. 1, where  $\beta = \infty$  and  $R$  is open circuited. Since  $V_{D1} = V_{BE1}$ , we have

$$V_1 = V_{E1}$$

Thus,

$$I_{D1} \times 40 = I_{E1} \times 2$$

$$\Rightarrow I_{D1} = 0.05 I_{E1}$$

But

$$I_{D1} = \frac{9 - 0.7}{80 + 40} = 0.069 \text{ mA} \simeq 0.07 \text{ mA}$$

Thus,

$$I_{E1} = \frac{0.069}{0.05} = 1.38 \text{ mA} \simeq 1.4 \text{ mA}$$

$$V_{E1} = I_{E1} \times 2 = 2.77 \text{ V} \simeq 2.8 \text{ V}$$

$$V_{B1} = V_{E1} + 0.7 = 3.5 \text{ V}$$

$$V_2 = 9 - I_{C1} \times 2 = 9 - 1.38 \times 2 \simeq 6.2 \text{ V}$$

$$V_{C1} = V_2 - V_{B2} = 6.2 - 0.7 = 5.5 \text{ V}$$

$$V_{E2} = V_2 = 6.2 \text{ V}$$

$$I_{E2} = \frac{9 - 6.2}{100 \Omega} = 28 \text{ mA}$$

$$I_{C2} = I_E = 28 \text{ mA}$$

$$V_{C2} = 28 \times 0.1 = 2.8 \text{ V}$$

**6.65**

(a) Consider first the case  $\beta = \infty$  and  $R$

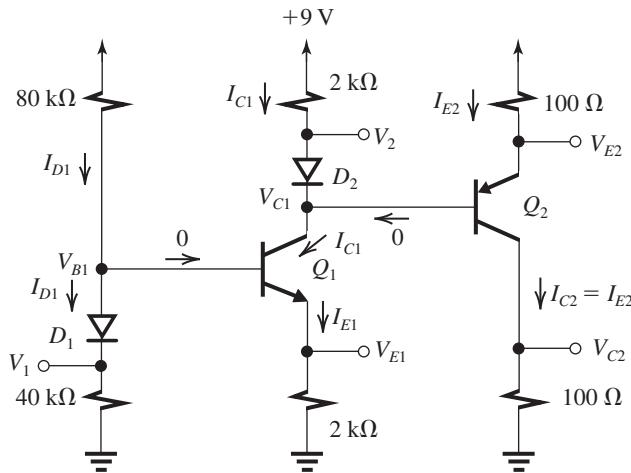


Figure 1  $\beta = \infty$ , and  $R$  is open circuited

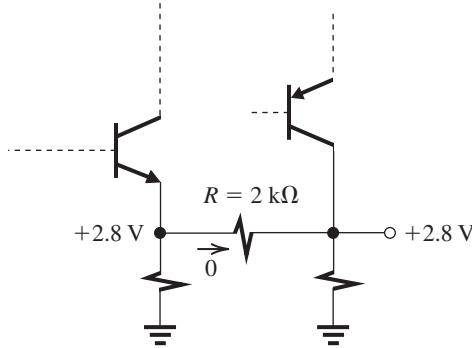


Figure 2

Now connecting the resistance  $R = 2 \text{ k}\Omega$  between  $C_1$  and  $E_2$  (see Fig. 2) both of which at 2.8 V, will result in zero current through  $R$ ; thus all voltages and currents remain unchanged.

(b) We next consider the situation with  $\beta = 100$ , first with  $R$  disconnected. The circuit is shown in Fig. 3.

Once again we observe that  $V_{E1} = V_1$ , thus

$$\begin{aligned} I_{E1} \times 2 &= I_{D1} \\ \Rightarrow I_{D1} &= 0.05I_{E1} \end{aligned}$$

The base current of  $Q_1$  is  $I_{E1}/101 \simeq 0.01I_{E1}$ .

Thus, the current through the 80-kΩ resistor is  $0.05I_{E1} + 0.01I_{E1} = 0.06I_{E1}$ , and

$$V_{B1} = V_{E1} + 0.7 = 2I_{E1} + 0.7$$

$$0.06I_{E1} = \frac{9 - V_{B1}}{80} = \frac{9 - (2I_{E1} + 0.7)}{80}$$

$$\Rightarrow I_{E1} = 1.22 \text{ mA}$$

$$V_{E1} = 1.22 \times 2 = 2.44 \text{ V}$$

$$V_{B1} = 2.44 + 0.7 = 3.14 \text{ V}$$

$$I_{C1} = \alpha I_{E1} = 0.99 \times 1.22 = 1.21 \text{ mA}$$

Observing that  $V_{E2} = V_2$ , we see that the voltage drops across the 2-kΩ resistor and the 100-Ω resistor are equal, thus

$$I_{D2} \times 2 = I_{E2} \times 0.1$$

$$\Rightarrow I_{D2} = 0.05I_{E2}$$

As the base current of  $Q_2$  is approximately  $0.01I_{E2}$ , a node equation at  $C_1$  yields

$$I_{D2} = I_{C1} - 0.01I_{E2}$$

Thus,

$$0.05I_{E2} = I_{C1} - 0.01I_{E2}$$

$$\Rightarrow 0.06I_{E2} = I_{C1}$$

$$I_{E2} = \frac{I_{C1}}{0.06} = \frac{1.21}{0.06} = 20.13 \text{ mA}$$

$$I_{D2} = 0.05 \times 20.13 = 1 \text{ mA}$$

$$V_{C1} = 9 - 1 \times 2 - 0.7 = 6.3 \text{ V}$$

$$V_{E2} = 6.3 + 0.7 = 7 \text{ V}$$

$$I_{C2} = \alpha I_{E2} = 0.99 \times 20.13 = 20 \text{ mA}$$

$$V_{C2} = 20 \times 0.1 = 2 \text{ V}$$

Finally, with the resistance  $R$  connected between  $E_1$  and  $E_2$ , it will conduct a current that we can initially estimate as

$$I = \frac{V_{E1} - V_{C2}}{R} = \frac{2.44 - 2}{2} = 0.22 \text{ mA}$$

This is a substantial amount compared to  $I_{E1} = 1.22 \text{ mA}$ , requiring that we redo the analysis with  $R$  in place. The resulting circuit is shown in Fig. 4.

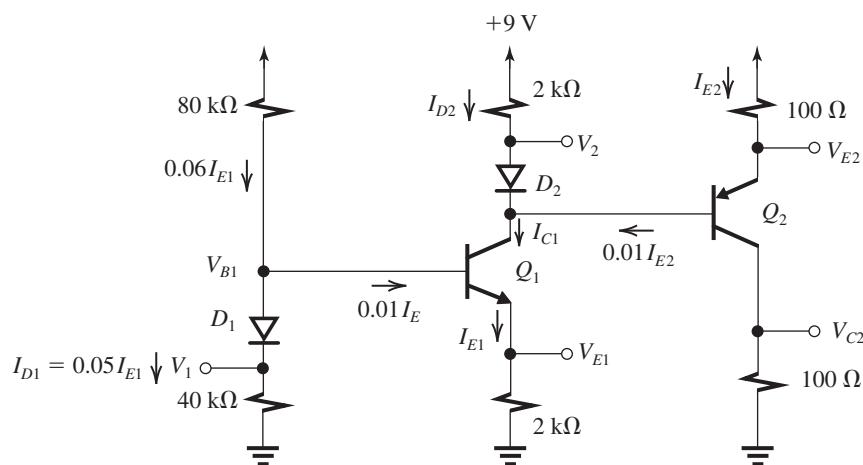


Figure 3

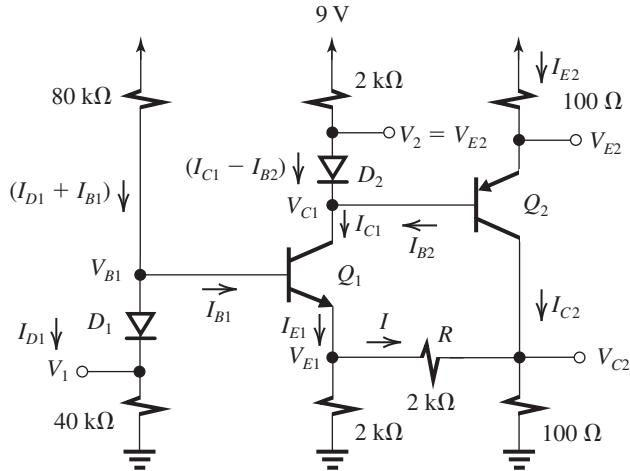


Figure 4

Denoting the emitter voltage of  $Q_1$ ,  $V_{E1}$ , and the current through  $R$  as  $I$ , the analysis proceeds as follows:

**Assignment Project Exam Help**

$$I_{D1} = \frac{V_1}{40} = \frac{V_{E1}}{40} = 0.025V_{E1}$$

$$I_{E1} = \frac{V_{E1}}{2} + I = 0.5V_{E1} + I$$

$$I_{B1} = \frac{I_{E1}}{101} = 0.005V_{E1} + 0.01I$$

$$I_{80\text{ k}\Omega} = I_{D1} + I_{B1} = 0.03V_{E1} + 0.01I$$

$$V_{C2} = V_{E1} - I \times 2 = V_{E1} - 2I$$

$$I_{C2} = -I + \frac{V_{C2}}{0.1} = 10V_{E1} - 21I$$

$$I_{B2} = \frac{I_{C2}}{101} = 0.1V_{E1} - 0.21I$$

$$I_{C1} = \alpha I_{E1} = 0.495V_{E1} + 0.99I$$

$$I_{D2} = I_{C1} - I_{B2} = 0.395V_{E1} + 1.2I$$

$$I_{E2} = \frac{I_{C2}}{\alpha} = 10.1V_{E1} - 21.2I$$

$$I_{D2} \times 2 = I_{E2} \times 0.1$$

$$2(0.395V_{E1} + 1.2I) = 0.1(10.1V_{E1} - 21.2I)$$

$$\Rightarrow I = 0.05V_{E2}$$

$$\text{Voltage drop across } 80\text{-k}\Omega \text{ resistor} = (0.03V_{E1} + 0.01I) \times 80 = 9 - V_{E1} - 0.7$$

$$\text{Substituting } I = 0.05V_{E2} \text{ gives}$$

$$V_{E1} = 2.41 \text{ V}$$

$$I = 0.12 \text{ mA}$$

Substituting these quantities in the equations above gives

$$V_{B1} = 2.41 + 0.7 = 3.11 \text{ V}$$

$$I_{E1} = 1.325 \text{ mA}$$

$$I_{C1} = 1.31 \text{ mA}$$

$$I_{D1} = 1.09 \text{ mA}$$

$$V_{C1} = 9 - 1.09 \times 2 - 0.7 = 6.12 \text{ V}$$

$$V_{E2} = 6.82 \text{ V}$$

$$I_{P2} = \frac{9 - 6.82}{0.1} = 21.8 \text{ mA}$$


$$I_{C2} = 0.99 \times 21.8 = 21.6 \text{ mA}$$

$$V_{C2} = 2.17 \text{ V}$$


### 6.66 (a) $\beta = \infty$

The analysis and results are given in the circuit diagram in Fig. 1 on page 27. The circled numbers indicate the order of the analysis steps.

### (b) $\beta = 100$

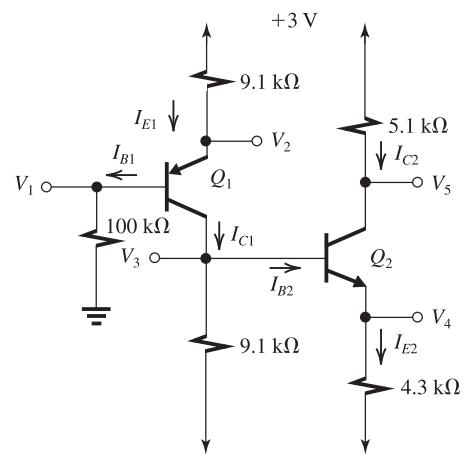Figure 2 ( $\beta = 100$ )

This figure belongs to Problem 6.66, part (a).

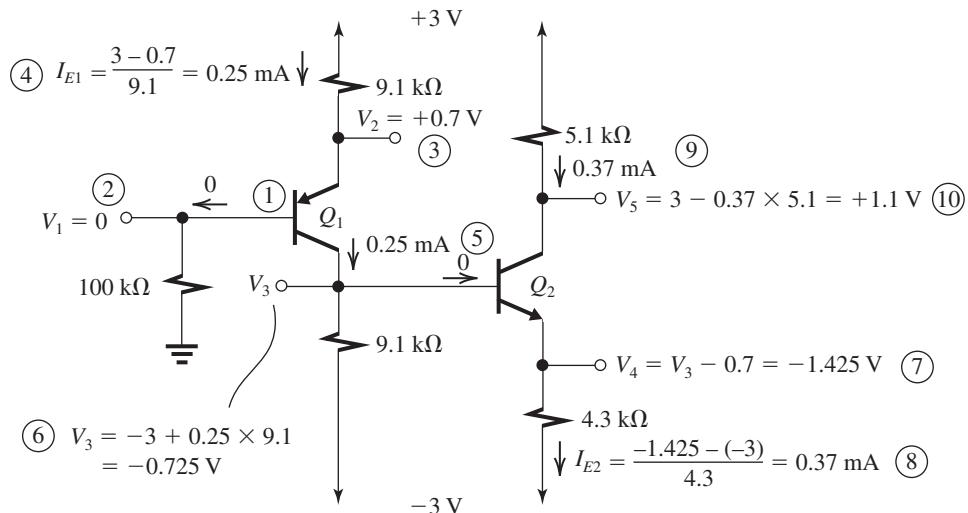Figure 1 ( $\beta = \infty$ )

By reference to Fig. 2 on page 26, we can write an equation for the loop containing the EBJ of Q<sub>1</sub> as follows:

$$3 = I_{E1} \times 9.1 + 0.7 + I_{B1} \times 100$$

Substituting  $I_{B1} = I_E / (\beta + 1) = I_E / 101$  and rearranging, we obtain

$$I_{E1} = \frac{3 - 0.7}{9.1 + \frac{100}{101}} = 0.228 \text{ mA}$$

Thus,

$$I_{B1} = \frac{I_{E1}}{101} = 0.0023 \text{ mA}$$

$$V_2 = V_1 + 0.7 = 0.93 \text{ V}$$

$$I_{C1} = \alpha I_{E1} = 0.99 \times 0.228 = 0.226 \text{ mA}$$

Then we write a node equation at C<sub>1</sub>:

$$I_{C1} = I_{B2} + \frac{V_3 - (-3)}{9.1}$$

Substituting for  $I_{C1} = 0.226 \text{ mA}$ ,  $I_{B2} = I_{E2}/101$ , and  $V_3 = V_4 + 0.7 = -3 + I_{E2} \times 4.3 + 0.7$  gives

$$0.226 = \frac{I_{E2}}{101} + \frac{-3 + 4.3I_{E2} + 0.7 + 3}{9.1}$$

$$= \frac{I_{E2}}{101} + \frac{4.3I_{E2}}{9.1} + \frac{0.7}{9.1}$$

$$\Rightarrow I_{E2} = 0.31 \text{ mA}$$

$$I_{B2} = 0.0031$$

$$I_{C1} - I_{B2} = 0.226 - 0.0031 = 0.223 \text{ mA}$$

$$V_3 = -3 + 0.223 \times 9.1 = -0.97 \text{ V} \simeq -1 \text{ V}$$

$$V_4 = V_3 - 0.7 = -1.7 \text{ V}$$

$$I_{C2} = \alpha I_{E2} = 0.99 \times 0.31 = 0.3 \text{ mA}$$

$$V_5 = +3 - 0.3 \times 5.1 = +1.1 \text{ V}$$

**6.67** Figure 1 on page 28 shows the circuit with  $\beta = \infty$ ; the required voltage values are indicated. The resistor values are obtained as follows:

$$V_2 = -0.7 \text{ V}$$

$$R_1 = \frac{V_2 - (-5)}{0.5 \text{ mA}}$$

$$\Rightarrow R_1 = 8.6 \text{ k}\Omega$$

$$R_2 = \frac{5 - V_3}{0.5} = \frac{5 - 0}{0.5} = 10 \text{ k}\Omega$$

$$V_4 = 0 + 0.7 = 0.7 \text{ V}$$

$$R_3 = \frac{5 - V_4}{0.5} = \frac{5 - 0.7}{0.5} = 8.6 \text{ k}\Omega$$

$$R_4 = \frac{V_5 - (-5)}{0.5} = \frac{-2 + 5}{0.5} = 6 \text{ k}\Omega$$

$$V_6 = V_5 - 0.7 = -2 - 0.7 = -2.7 \text{ V}$$

$$R_6 = \frac{V_6 - (-5)}{1} = \frac{-2.7 + 5}{1} = 2.3 \text{ k}\Omega$$

$$R_5 = \frac{5 - V_7}{1} = \frac{5 - 1}{1} = 4 \text{ k}\Omega$$

Consulting the table of 5% resistors in Appendix J, we select the following resistor values:

$$R_1 = 8.2 \text{ k}\Omega \quad R_2 = 10 \text{ k}\Omega \quad R_3 = 10 \text{ k}\Omega$$

$$R_4 = 6.2 \text{ k}\Omega \quad R_5 = 3.9 \text{ k}\Omega \quad R_6 = 2.4 \text{ k}\Omega$$

The circuit with the selected resistor values is shown in Fig. 2. Analysis of the circuit proceeds as follows:

$$V_2 = -0.7 \text{ V}$$

This figure belongs to Problem 6.67.

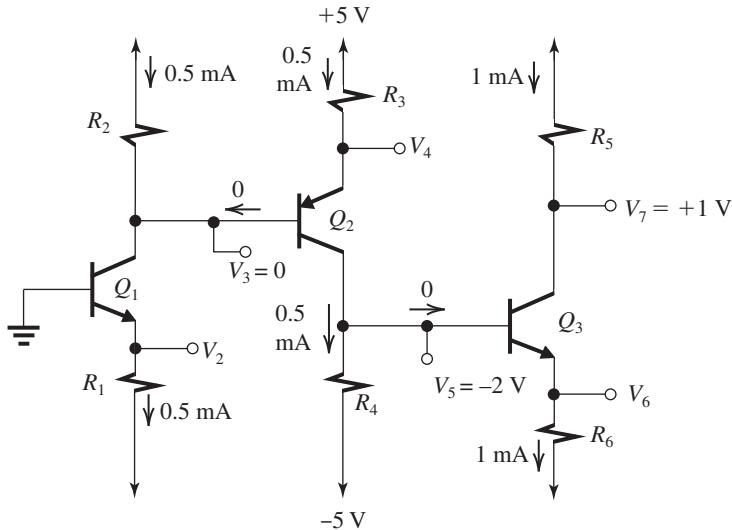


Figure 1

This figure belongs to Problem 6.67.

## Assignment Project Exam Help

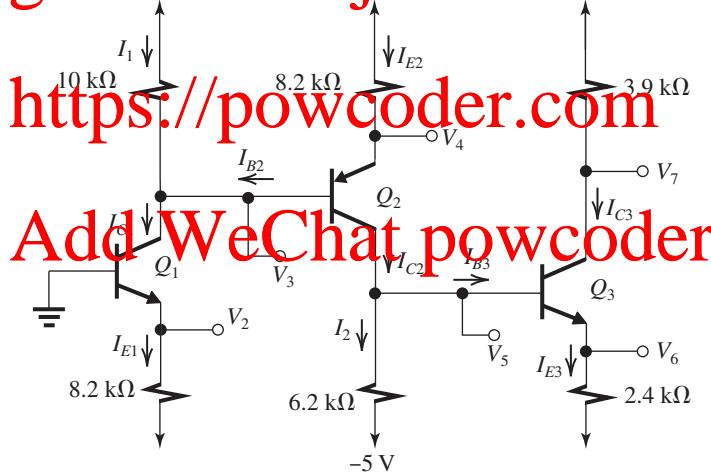


Figure 2

$$I_{E1} = \frac{V_2 - (-5)}{8.2} = \frac{-0.7 + 5}{8.2} = 0.524 \text{ mA}$$

$$\Rightarrow I_{E2} = 0.542 \text{ mA}$$

$$I_{C1} = \alpha I_{E1} = 0.99 \times 0.524 = 0.52 \text{ mA}$$

$$V_4 = 5 - 0.542 \times 8.2 = 0.56 \text{ V}$$

The current  $I_1$  through the 10-kΩ resistor is given by

$$V_3 = 0.56 - 0.7 = -0.14 \text{ V}$$

$$I_1 = I_{C1} - I_{B2} = I_{C1} - \frac{I_{E2}}{101}$$

$$I_{C2} = \alpha I_{E2} = 0.99 \times 0.542 = 0.537 \text{ mA}$$

Noting that the voltage drop across the 10-kΩ resistor is equal to  $(I_{E2} \times 8.2 + 0.7)$ , we can write

$$I_2 = I_{C2} - I_{B3} = 0.537 - \frac{I_{E3}}{101}$$

$$I_1 \times 10 = 8.2I_{E2} + 0.7$$

Since the voltage drop across the 6.2-kΩ resistor is equal to  $(0.7 + I_{E3} \times 2.4)$ ,

Thus,

$$I_2 \times 6.2 = 0.7 + 2.4I_{E3}$$

$$10\left(0.52 - \frac{I_{E2}}{101}\right) = 8.2I_{E2} + 0.7$$

$$6.2\left(0.537 - \frac{I_{E3}}{101}\right) = 0.7 + 2.4I_{E3}$$

$$\Rightarrow I_{E3} = 1.07 \text{ mA}$$

$$V_6 = -5 + 1.07 \times 2.4 = -2.43 \text{ V}$$

$$V_5 = V_6 + 0.7 = -1.73$$

$$I_{C3} = \alpha \times I_{E3} = 0.99 \times 1.07 = 1.06 \text{ mA}$$

$$V_7 = -3.9 \times 1.06 = 0.87 \text{ V}$$

**6.68** Refer to the circuit in Fig. P6.68.

- (a) For  $v_I = 0$ , both transistors are cut off and all currents are zero. Thus

$$V_B = 0 \text{ V} \quad \text{and} \quad V_E = 0 \text{ V}$$

- (b) For  $v_I = +2 \text{ V}$ ,  $Q_1$  will be conducting and  $Q_2$  will be cut off, and the circuit reduces to that in Fig. 1.

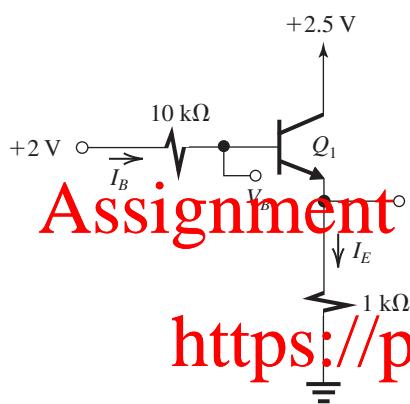


Figure 1

# Assignment Project Exam Help

# Add WeChat powcoder

Since  $V_B$  will be lower than  $+2 \text{ V}$ ,  $V_C$  will be higher than  $V_B$  and the transistor will be operating in the active mode. Thus,

$$I_E = \frac{2 - 0.7}{1 + \frac{10}{51}} = 1.1 \text{ mA}$$

$$V_E = +1.1 \text{ V}$$

$$V_B = 1.8 \text{ V}$$

- (c) For  $v_I = -2.5 \text{ V}$ ,  $Q_1$  will be off and  $Q_2$  will be on, and the circuit reduces to that in Fig. 2.

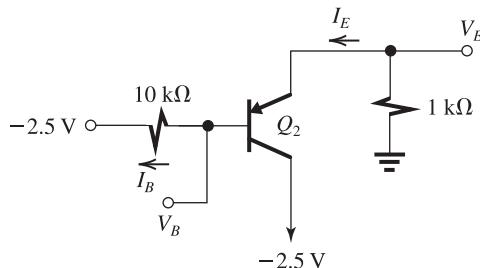


Figure 2

Since  $V_B > -2.5$ ,  $V_C$  will be lower than  $V_B$  and  $Q_2$  will be operating in the active region. Thus

$$I_E = \frac{2.5 - 0.7}{1 + \frac{10}{51}} = 1.5 \text{ mA}$$

$$V_E = -I_E \times 1 = -1.5 \text{ V}$$

$$V_B = -1.5 - 0.7 = -2.2 \text{ V}$$

- (d) For  $v_I = -5 \text{ V}$ ,  $Q_1$  will be off and  $Q_2$  will be on, and the circuit reduces to that in Fig. 3.

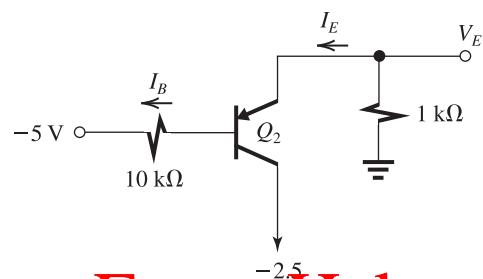


Figure 3

Here we do not know whether  $Q_2$  is operating in the active mode or in saturation. Assuming active-mode operation, we obtain

$$I_E = \frac{5 - 0.7}{1 + \frac{10}{51}} = 3.6 \text{ mA}$$

$$V_E = -3.6 \text{ V}$$

$$V_B = -4.3 \text{ V}$$

which is impossible, indicating that our original assumption is incorrect and that  $Q_2$  is saturated. Assuming saturation-mode operation, we obtain

$$V_E = V_C + V_{ECsat} = -2.5 + 0.2 = -2.3 \text{ V}$$

$$I_E = \frac{-V_E}{1 \text{ k}\Omega} = 2.3 \text{ mA}$$


$$V_B = V_E - 0.7 = -3 \text{ V}$$

$$I_B = \frac{-3 - (-5)}{10} = 0.2 \text{ mA}$$


$$I_C = I_E - I_B = 2.3 - 0.2 = 2.1 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = \frac{2.1}{0.2} = 10.5$$

which is lower than  $\beta$ , verifying that  $Q_2$  is operating in saturation.

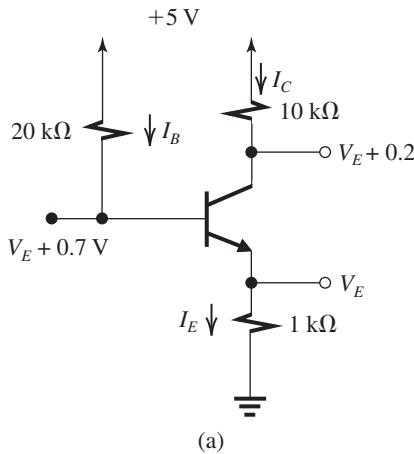**6.69 (a)**

(a)

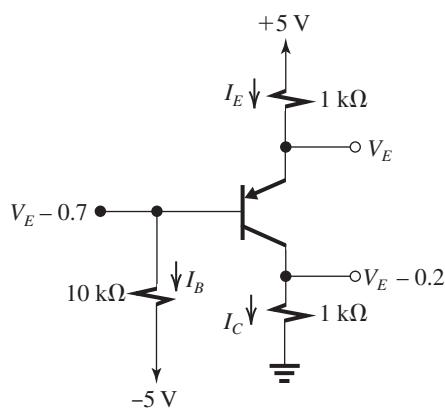**(b)**

(b)

Assuming saturation-mode operation, the terminal voltages are interrelated as shown in the figure, which corresponds to Fig. P6.69(a). Thus we can write

$$I_E = \frac{V_E}{5} = V_E$$

$$I_C = \frac{5 - (V_E + 0.2)}{10} = 0.5 - 0.1(V_E + 0.2)$$

$$I_B = \frac{5 - (V_E + 0.7)}{20} = 0.15 - 0.05(V_E + 0.7)$$

Now, imposing the constraint

$$I_E = I_C + I_B$$

# Assignment Project Exam Help

results in

$$V_E = 0.5 - 0.1(V_E + 0.2) + 0.25 - 0.05(V_E + 0.7)$$

$$\Rightarrow V_E = 0.6 \text{ V}$$

$$V_C = 0.8 \text{ V}$$

$$V_B = 1.3 \text{ V}$$

$$I_C = \frac{5 - 0.8}{10} = 0.42 \text{ mA}$$

$$I_B = \frac{5 - 1.3}{20} = 0.185 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{0.42}{0.185} = 2.3$$

which is less than the value of  $\beta_1$  verifying saturation-mode operation.

Assuming saturation-mode operation, the terminal voltages are interrelated as shown in the figure, which corresponds to Fig. P6.69(b). We can obtain the currents as follows:

$$I_E = \frac{5 - V_E}{5} = V_E$$

$$I_C = \frac{V_E - 0.2}{1} = V_E - 0.2$$

$$I_B = \frac{V_E - 0.7 - (-5)}{10} = 0.1 V_E + 0.43$$

Imposing the constraint

$$I_E = I_B + I_C$$

results in

$$5 - V_E = V_E - 0.2 + 0.1 V_E + 0.43$$

$$\Rightarrow V_E = +2.27 \text{ V}$$

$$V_C = +2.07 \text{ V}$$

$$V_B = 1.57 \text{ V}$$


$$I_C = \frac{2.07}{1} = 2.07 \text{ mA}$$

$$I_B = \frac{1.57 - (-5)}{10} = 0.657 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = \frac{2.07}{0.657} = 3.2$$

which is lower than the value of  $\beta$ , verifying saturation-mode operation.

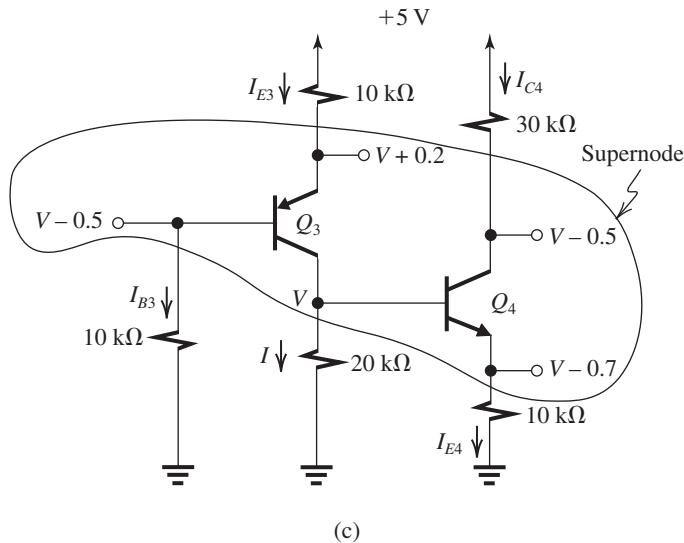This figure belongs to Problem 6.69, part (c).



(c)

(c) We shall assume that both  $Q_3$  and  $Q_4$  are operating in saturation. To begin the analysis shown in the figure, which corresponds to Fig. P6.69(c), we denote the voltage at the emitter of  $Q_3$  as  $V$  and then obtain the voltages at all other nodes in terms of  $V$ , utilizing the fact that a saturated transistor has  $|V_{CE}| = 0.2$  V and of course  $|V_{BE}| = 0.7$  V. Note that the choice of the collector node to begin the analysis is arbitrary; we could have selected any other node and denoted its voltage as  $V$ . We next draw a circle around the two transistors to define a "supernode". A node equation for the supernode will be

$$I_{E3} + I_{C4} = I_{B3} + I + I_{E4} \quad (1)$$

where

$$I_{E3} = \frac{5 - (V + 0.2)}{10} = 0.48 - 0.1V \quad (2)$$

$$I_{C4} = \frac{5 - (V - 0.5)}{30} = 0.183 - 0.033V \quad (3)$$

$$I_{B3} = \frac{5 - (V - 0.5)}{10} = 0.1V - 0.05 \quad (4)$$

$$I = \frac{V}{20} = 0.05V \quad (5)$$

$$I_{E4} = \frac{V - 0.7}{10} = 0.1V - 0.07 \quad (6)$$

Substituting from Eqs. (2)–(6) into Eq. (1) gives

$$\begin{aligned} & 0.48 - 0.1V + 0.183 - 0.033V \\ & = 0.1V - 0.05 + 0.05V + 0.1V - 0.07 \\ & \Rightarrow V = 2.044 \text{ V} \end{aligned}$$

Thus

$$V_C4 = V - 0.5 = 1.54 \text{ V}$$

Next we determine all currents utilizing Eqs. (1)–(6).

$$I_{E3} = 0.276 \text{ mA } I_{C4} = 0.116 \text{ mA}$$

$$I_{B3} = 0.154 \text{ mA } I = 0.01 \text{ mA}$$

$$I_{E4} = 0.134$$

The base current of  $Q_4$  can be obtained from

$$I_{B4} = I_{E4} - I_{C4} = 0.134 - 0.116 = 0.018 \text{ mA}$$

Finally, the collector current of  $Q_3$  can be found as

$$I_{C3} = I + I_{B4} = 0.102 + 0.018 = 0.120$$

The forced  $\beta$  values can now be found as

$$\beta_{\text{forced}3} = \frac{I_{C3}}{I_{B3}} = \frac{0.120}{0.154} = 0.8$$

$$\beta_{\text{forced}4} = \frac{I_{C4}}{I_{B4}} = \frac{0.116}{0.018} = 6.4$$

Both  $\beta_{\text{forced}}$  values are well below the  $\beta$  value of 50, verifying that  $Q_3$  and  $Q_4$  are in deep saturation.